


KSETA chip design course


Ivan Peric, Toko Hirono





- Link to the lecture design of analogue circuits 2022/23
- https://ilias.studium.kit.edu/ilias.php?ref_id=1926247&cmd=view&cmdClass=ilrepositorygui&cmdNode=x1&baseClass=ilrepositorygui
- (Everyone can join the ILAS course)
- Link to older lectures (English/German)
- <https://adl.ipe.kit.edu/english/28.php>


- Behzad Razavi:
- Design of Analog CMOS Integrated Circuits
- Fundamentals of Microelectronics
- RF Microelectronics
- Design of CMOS phase locked loops

Introduction

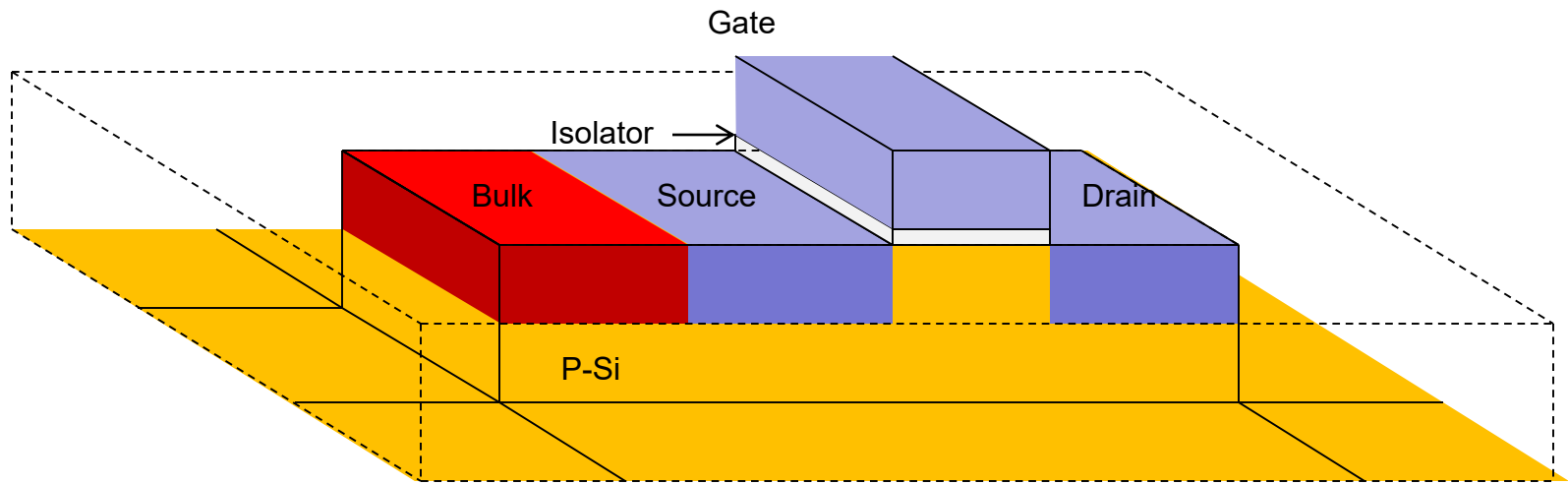

 

 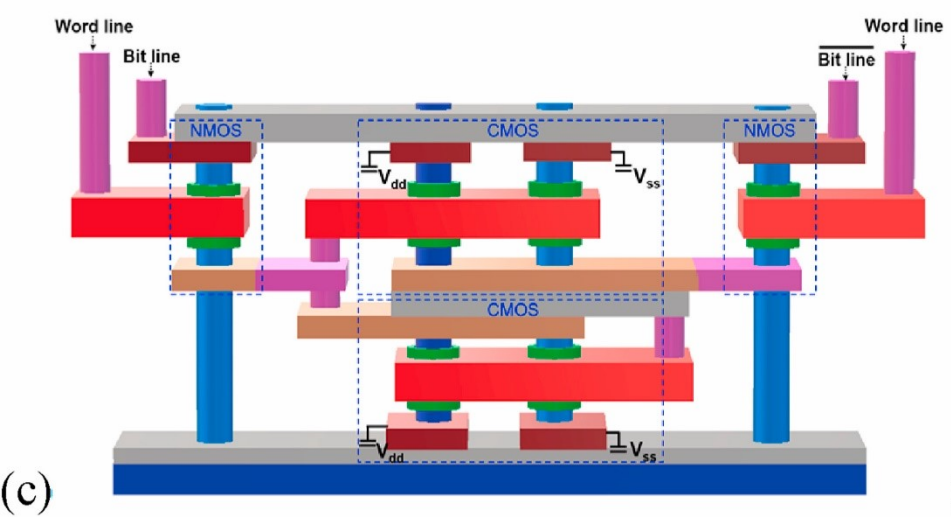 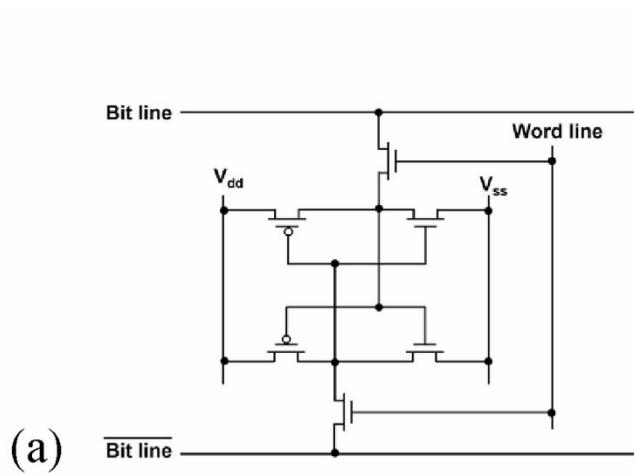


 

Fotomaske




Projektor (stepper)





 


Wafer




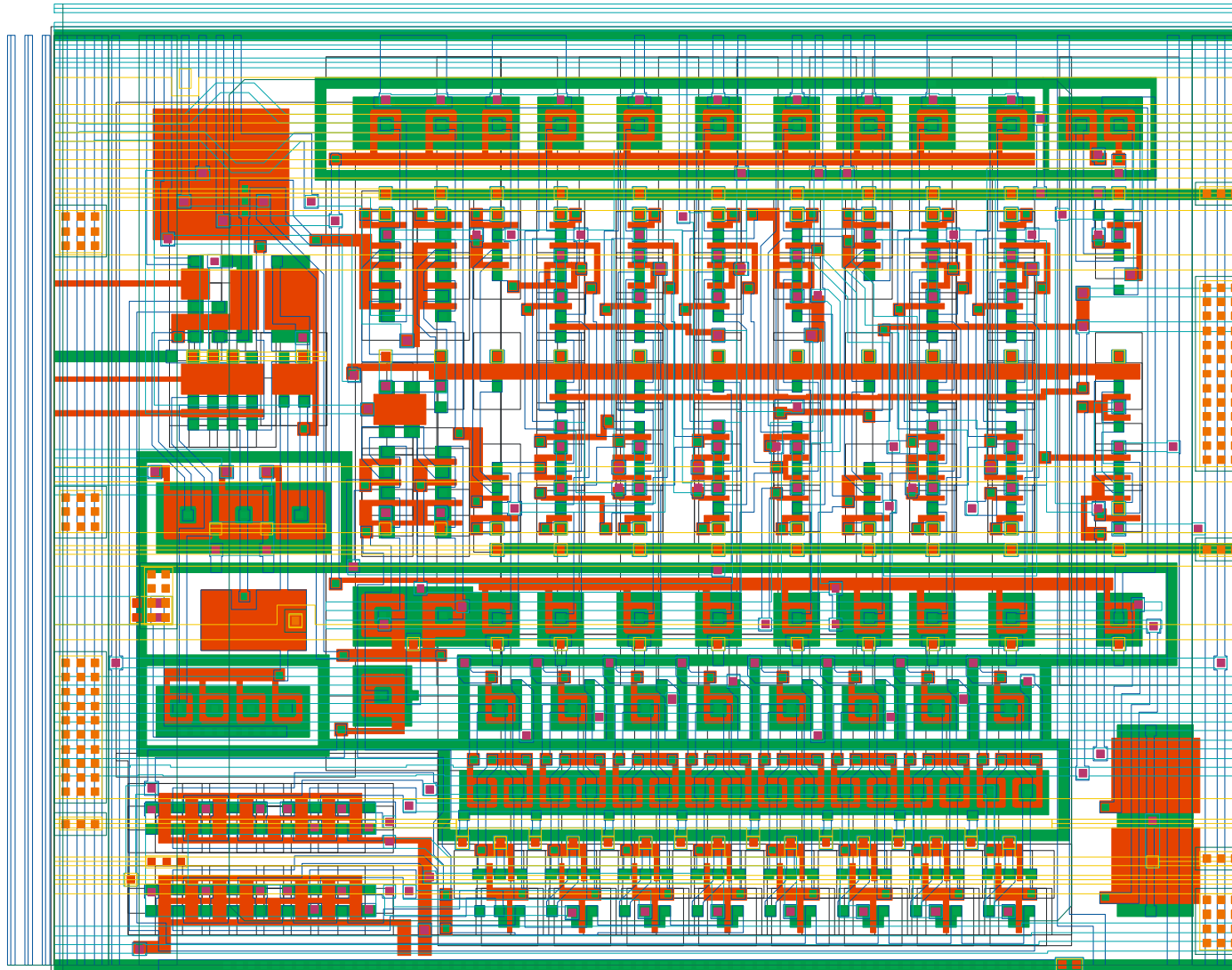






Digital design flow

     



Analog design flow

 

Digital design flow

     

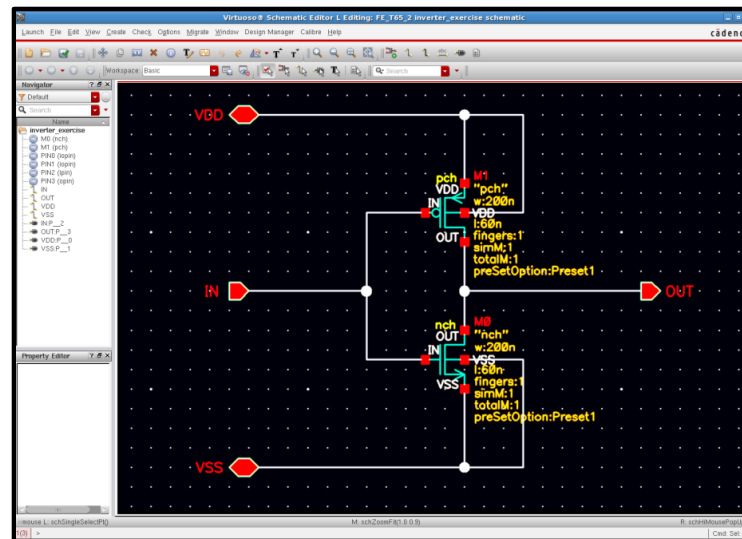


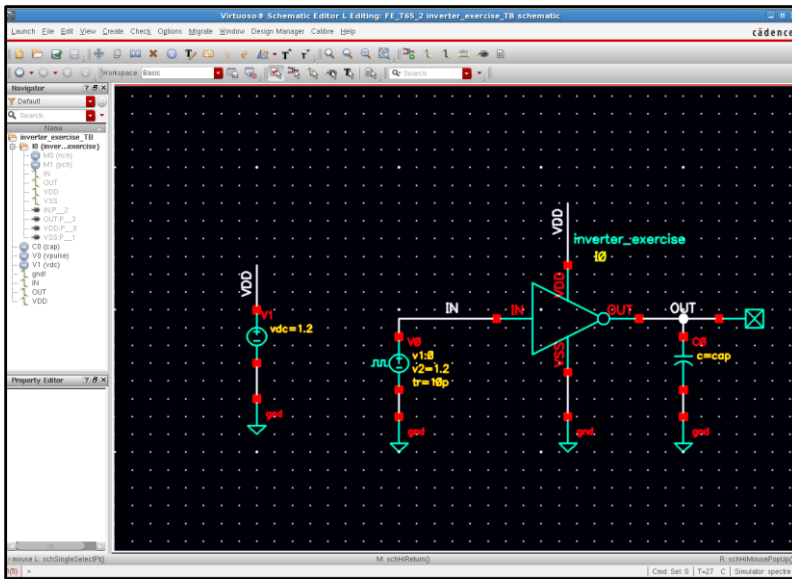

Test	Output	Normal	Spec	Weight	Pass/Fail
FE_T65_2_inverter_exercise_TB_1_IN					
FE_T65_2_inverter_exercise_TB_1_OUT					
FE_T65_2_inverter_exercise_TB_1_Pwr					4.150p
FE_T65_2_inverter_exercise_TB_1_L_Lvl					0.530p
FE_T65_2_inverter_exercise_TB_1_POWER					273.0p
FE_T65_2_inverter_exercise_TB_1_ABVDD					

Design Variables	Name	Value
with_p		
c=cap		

Analysis	Item	Repeat	Expr	Value	Plot	Save	Save Options
Outputs	IN				<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	altv
	OUT				<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	altv
	L_Lvl				<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
	POWER				<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
	AVDD				<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	

 

Virtuoso® Layout Suite L Reading: CORELIB_HV INVX4_HV layout

Launch File Edit View Create Verify Connectivity Options Tools Window Assura Quantus Calibre Help

Classic

(F)Select:0 Sel(N):0 Sel(I):0 Sel(O):0 X 4.200 Y 7.400 dX -14.500

Palette

Layers

default

Valid Used Routing

Filter Filter

NW drawing

AV NV AS NS

Layer	Purpo...	V	S
RX	drw	✓	✓
DN	drw	✓	✓
NW	drw	✓	✓
PC	drw	✓	✓
BP	drw	✓	✓
CA	drw	✓	✓
M1	drw	✓	✓
M1	pin	✓	✓
M1	label	✓	✓
SXCUT	label	✓	✓
GRLOGIC	drw	✓	✓
text	drw	✓	✓


Objects

Objects	V	S
Instances	✓	✓
Pins	✓	✓
Vias	✓	✓

Objects Grids

mouse L: mgc_calibre_realtime_Btn1Down() mouseSingleSelectPt()_leiLMBPress() M: hiZoomAbsoluteScale(hiGetCurrentWindow() 0.9) R: _IxHiMousePopUp()

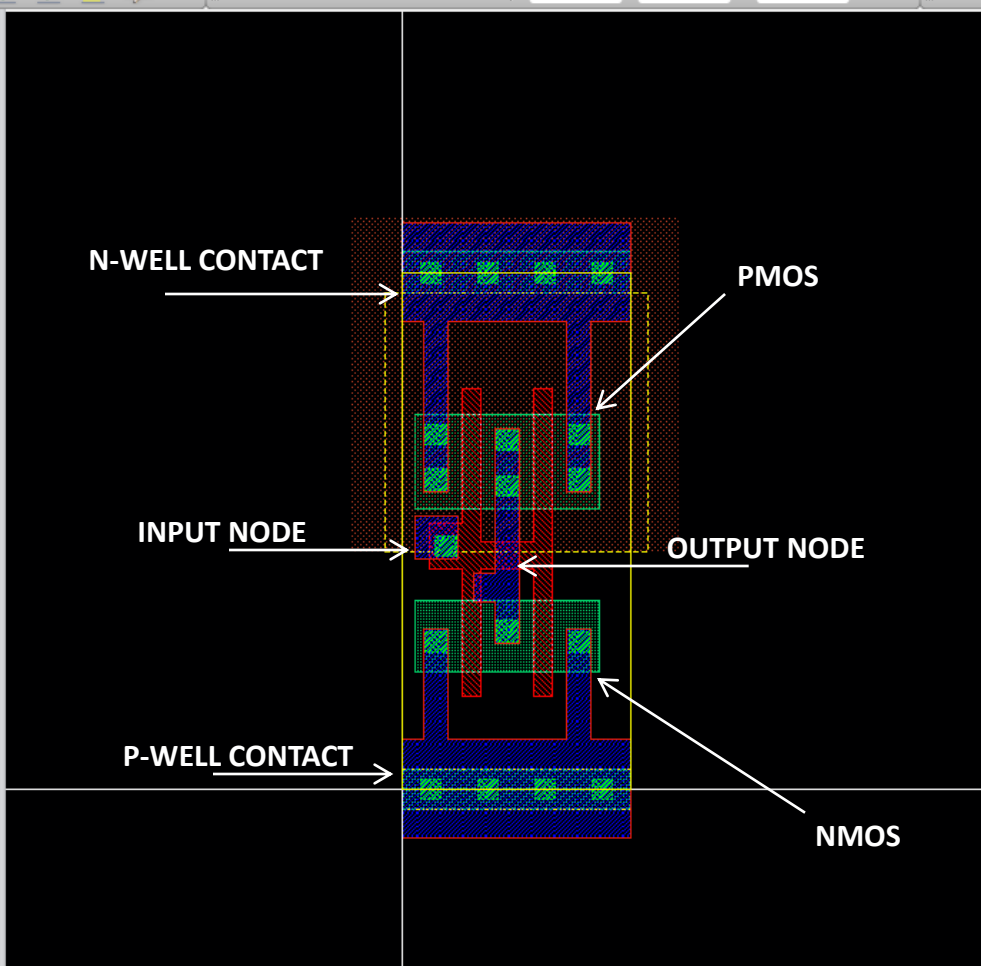11(12) hitkit: ams_4.11 Tech: h18a7 User: iperic Cmd: █



The diagram shows a cross-sectional view of a CMOS transistor layout. The central region is the **INPUT NODE**, which is connected to the **OUTPUT NODE**. The **N-WELL CONTACT** is located at the top, and the **P-WELL CONTACT** is at the bottom. The **PMOS** transistor is formed by the N-well and the input node, while the **NMOS** transistor is formed by the P-well and the input node. The layout includes various layers such as M1, M2, and M3, and is displayed in the Virtuoso Layout Suite L Reading environment.


```

module ADC_digital_v (
input comp_in,
input start,clk,rst_n,
output [7:0] dig_val,
output sample,
output sampleb,
output eoc,
output reg [7:0] dig_val_reg
);

```

```

reg [9:0] sreg;
reg [7:0] dacreg;
assign sample = sreg[9];
assign sampleb = ~sreg[9];
assign eoc = sreg[0];
assign dig_val = dacreg;
wire reset;
assign reset = start;

```

```

always @(posedge clk or negedge rst_n) begin
if (~rst_n) begin

```

```

sreg <= 10'd0;
dacreg <= 8'd0;

```

```

end
else begin

```

```

sreg[9:0] <= {start,sreg[9:1]};
if(eoc) dig_val_reg <= dacreg;
if(reset == 1) dacreg[7:0] <= 0;
else dacreg[7:0] <= sreg[9:2] | ( (sreg[8:1] & {8{~comp_in}} ) | (~sreg[8:1] & dacreg[7:0]) );

```

```


end//no reset
end//alw

```

```

endmodule



```

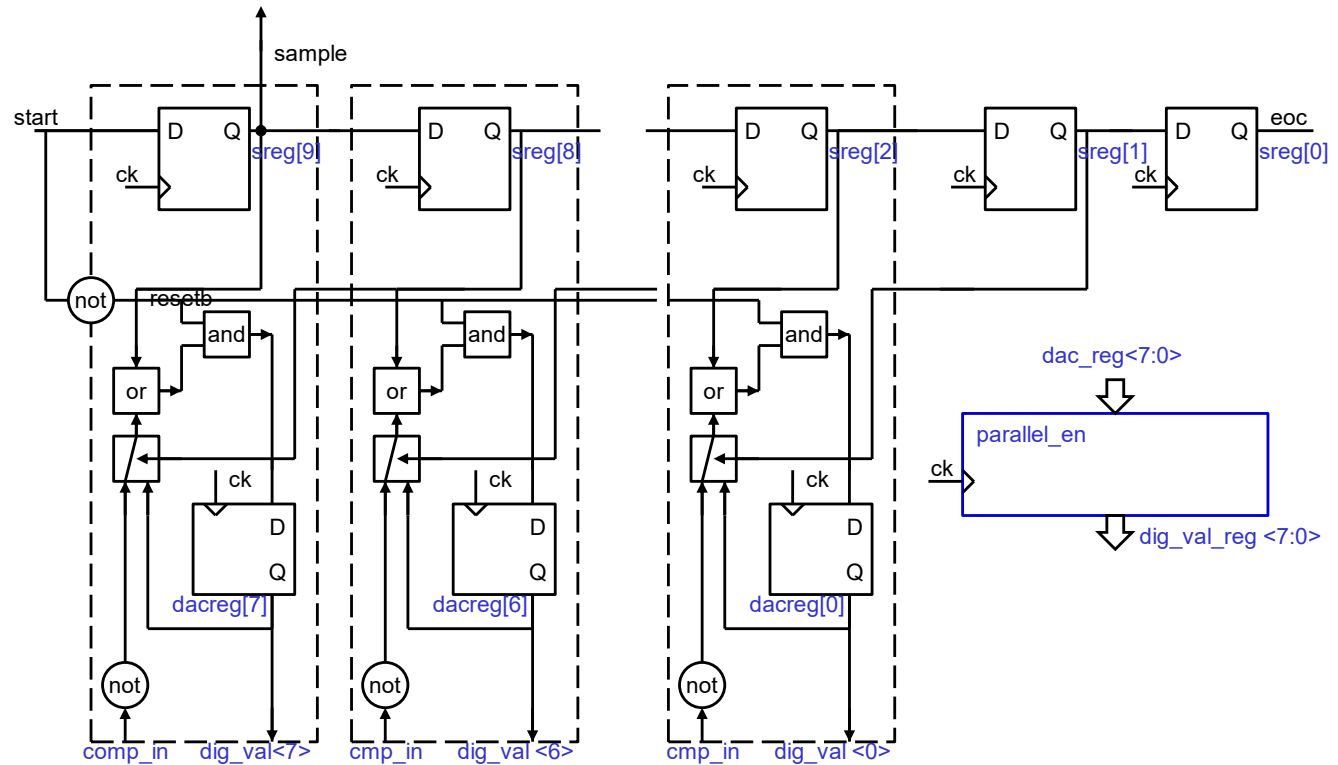



code that describes shift register


output register

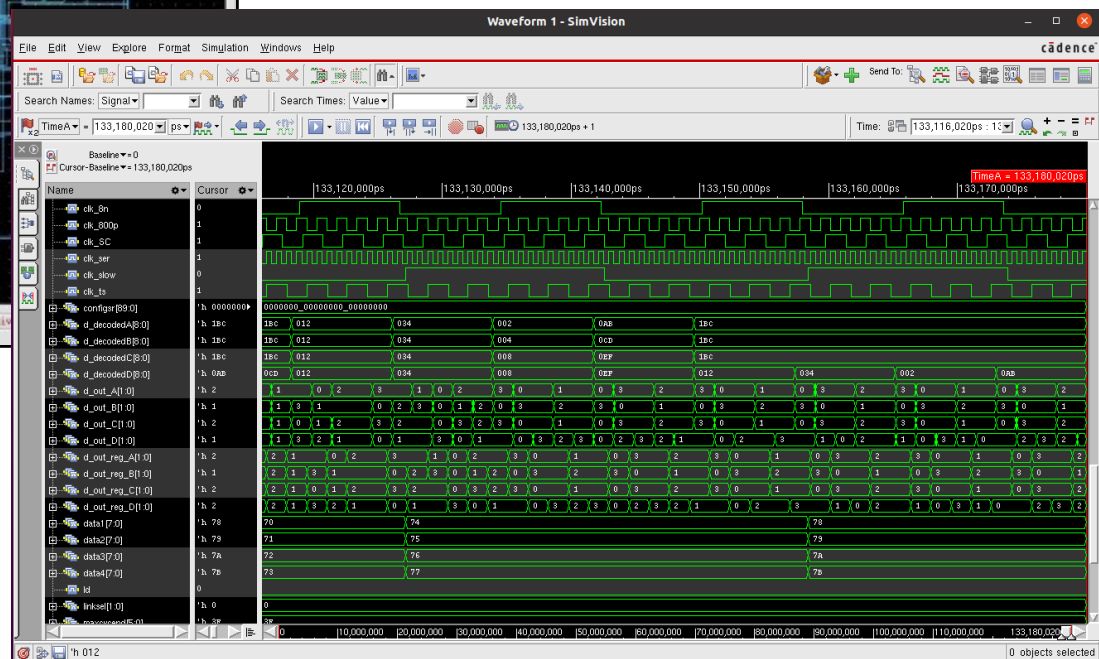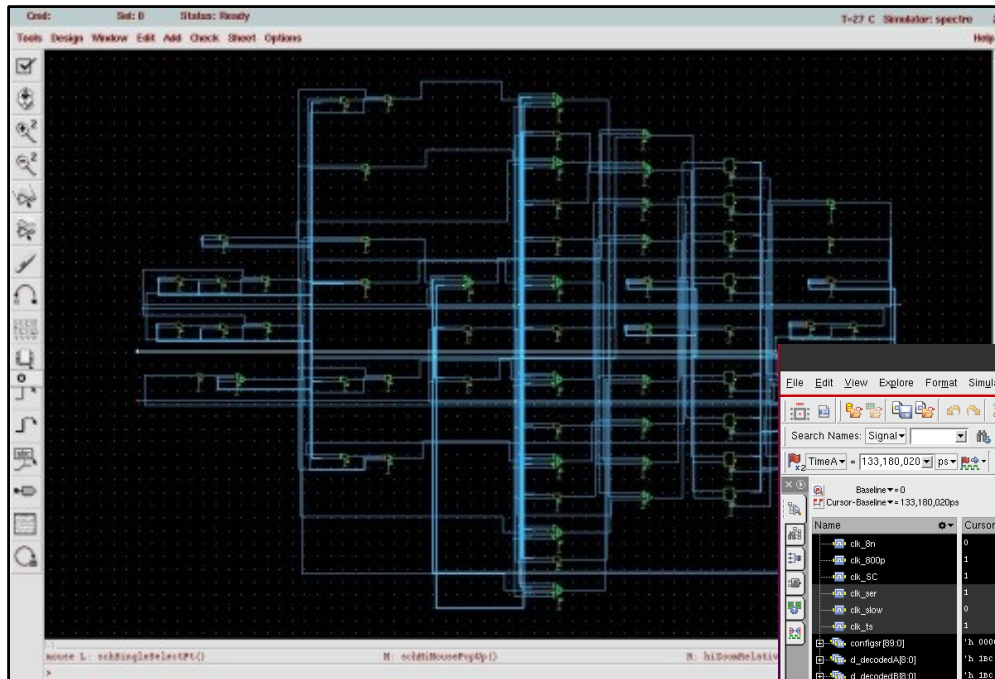Not very readable line with bitwise operations that describes the combinatorial connections between sreg and dacreg



Analog design flow

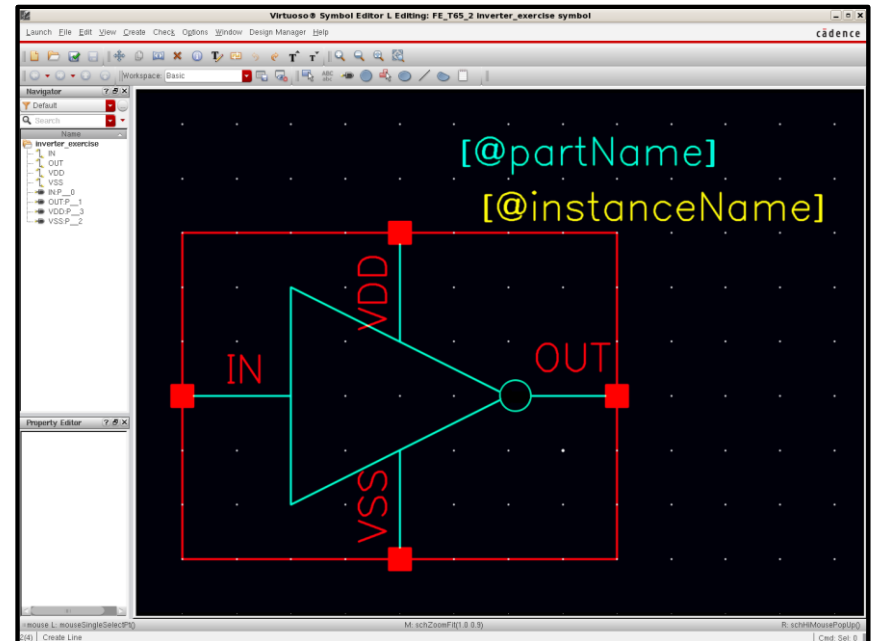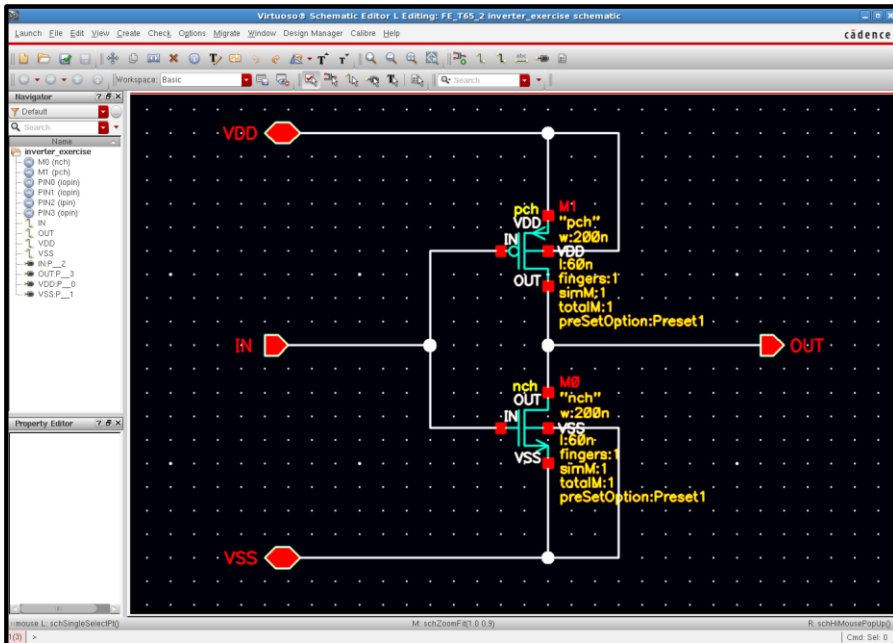




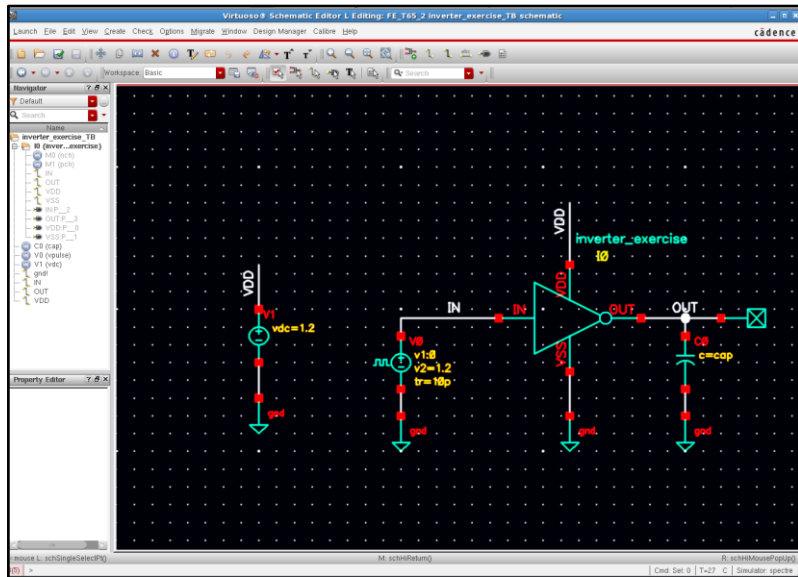



Test	Output	Monitor	Spec	Weight	Pass/Fail
FE_T65_2_inverter_exercise_TB_1 /IN	IN				
FE_T65_2_inverter_exercise_TB_1 /OUT	OUT				
FE_T65_2_inverter_exercise_TB_1 L_in	L_in		1.150p		
FE_T65_2_inverter_exercise_TB_1 L_out	L_out		6.530p		
FE_T65_2_inverter_exercise_TB_1 /POWER	POWER		273.0u		
FE_T65_2_inverter_exercise_TB_1 /AVDD	AVDD				

Design Variables	Value
with_2p	
width_p	
CNP	


Outputs	Monitor/Signal type	Value	Plot	Sim	Sim. Options
IN			all		all
OUT			all		all
L_in					
L_out					
POWER					
AVDD					

 

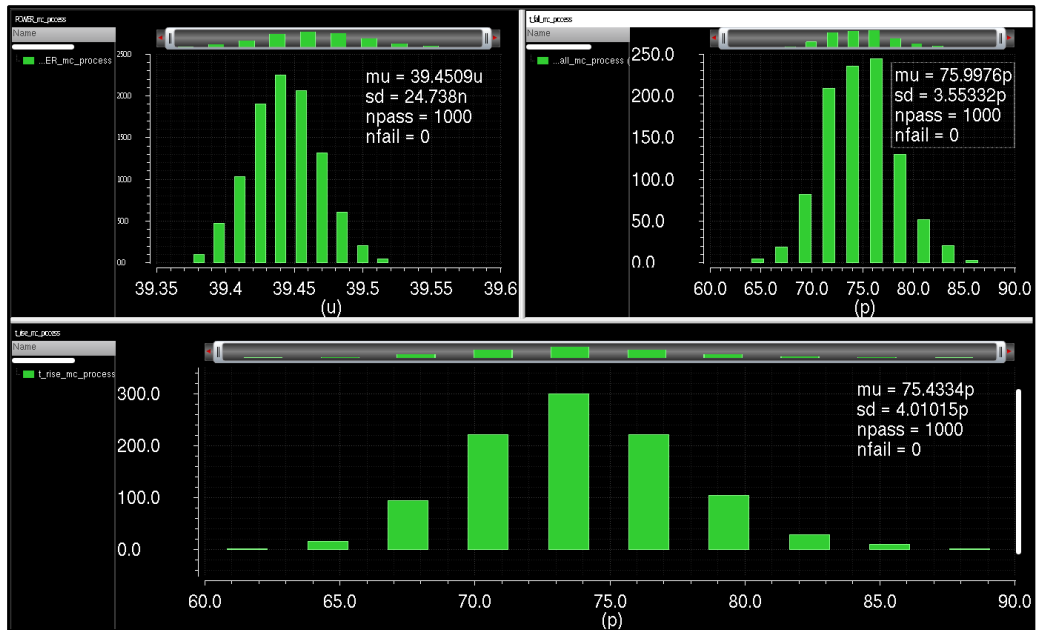  


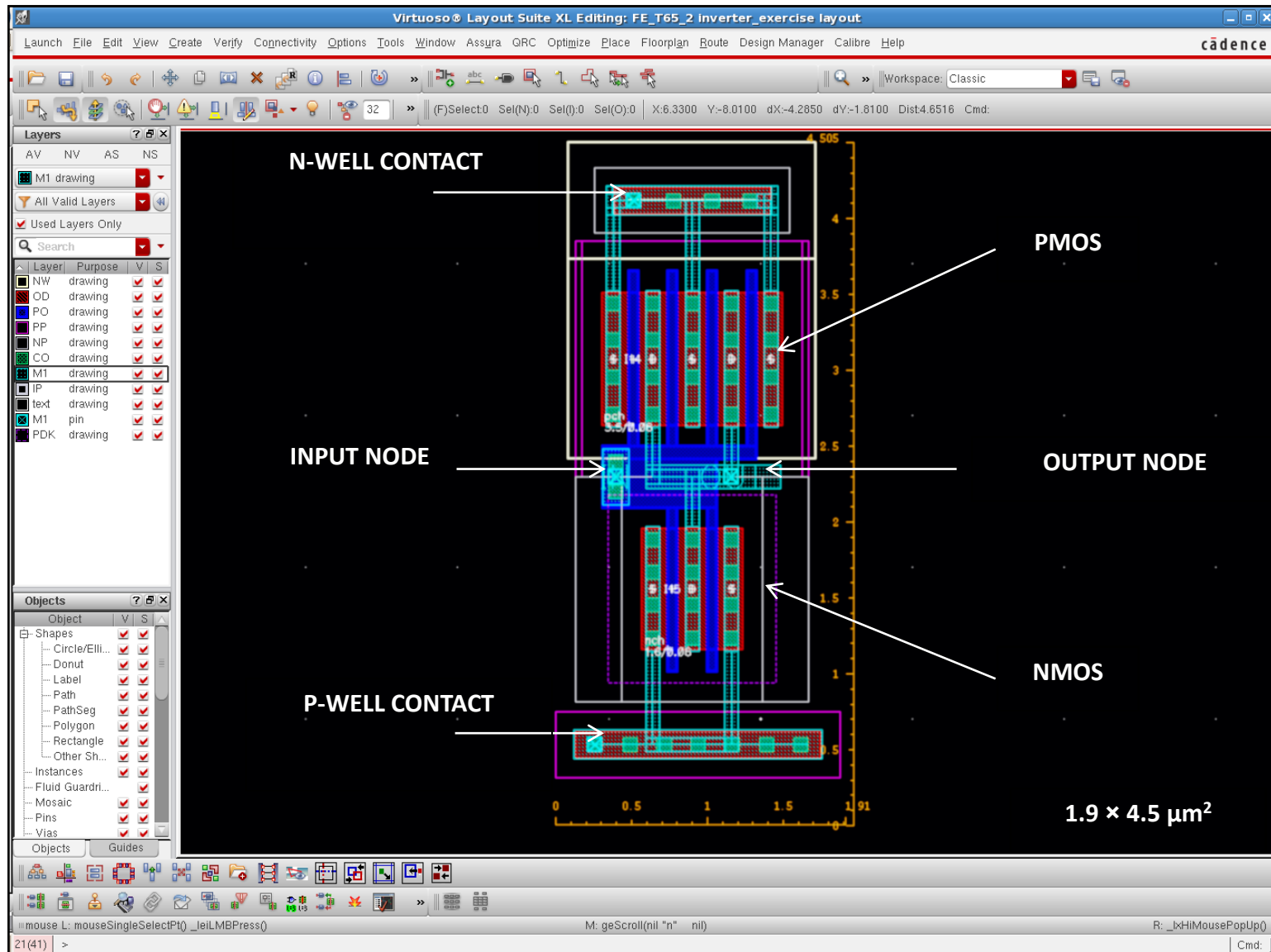



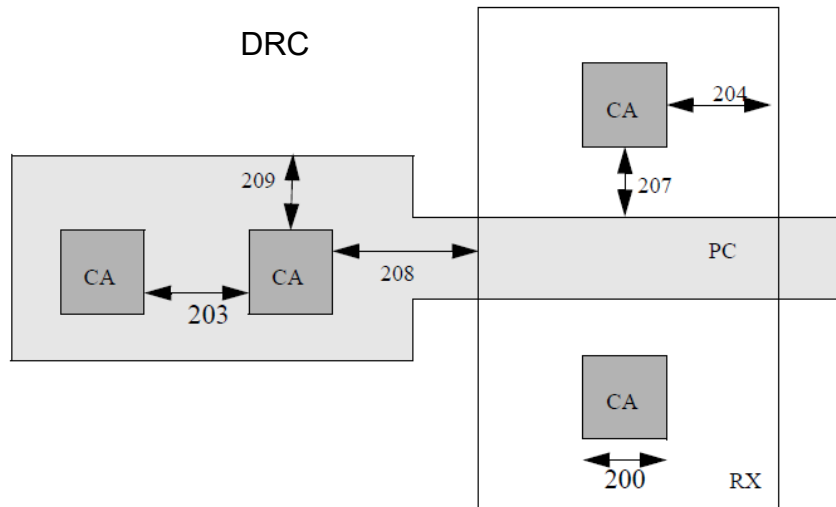
- Layout rules (part of PDK)
- DRC review of layout rules
- Avalanche Layout Schematic Comparison
- Layout -> Netlist <-> Netlist <- Schematic
- Extraction of capacities from layout
- Post-Layout Simulation
- Adaptation of the circuit diagram necessary



LVS

 


A basic cell: inverter

   

Views of a cell: Inverter.schematic Inverter.layout Inverter.symbol


Complex cell Controller

Uses basic schematic cells

 

Controller.schematic

Uses basic layout cells

 

Controller.layout

- In the case of analog circuits, the lowest level in the hierarchy contains the components: NMOS, PMOS transistor, capacitor, and resistor. These basic components are the instances (copies) of corresponding cells.
- In the case of digital circuits, the basic components are the instances of logical gates and the memory components (AND, OR, inverter, flip-flop).
- Although a chip has billions of transistors (billions of instances, copies), the number of cells is not large.

- Foundries and processes



UMC



TSMC

TSI semiconductors



Globalfoundries



Lfoundry




X-FAB Dresden





AMS

IHP

 - Opto CMOS, HVCMOS, SOI, BiCMOS
- FinFET, Fully Depleted SOI, nanowire Gate all around
- Process nodes:
- 0.35 μm , 0.18 μm , 0.13 μm , 0.11 μm , 90, 65, 55, 40, 28, 22, 16, 12, 7, 6, 5nm




<http://www.extremetech.com/>

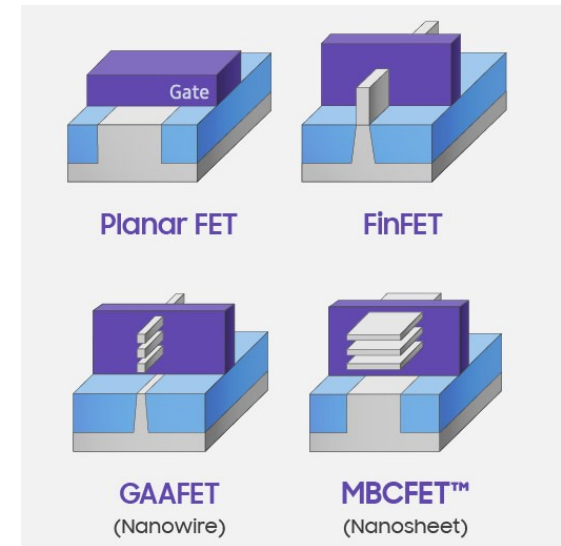
 


<https://www.cnx-software.com/2019/05/17/mbcfet-process-technology-3nm-processors/>

 
- Europractice: Multi Project Runs und Design Support
- <http://europractice-ic.com/>
- Offers:
- Foundry access
- Software download
- Software Licenses
- Engineering runs
- MPW runs
- <https://europractice-ic.com/mpw-prototyping/general/mpw-minisic/>
-



Engineering run

  


MPW run

 

Charge sensitive amplifier

- Charge sensitive amplifier (CSA) consists of a voltage amplifier (“amplifier-core”) with negative voltage amplification $-A$ and feedback circuit (capacitance C_f)
- Ideal CSA works as an integrator, the output voltage is integral of the input current multiplied by $1/C_f$
- Therefore, the ideal CSA has the charge amplification
- $A_Q = \frac{V_{out,max}}{Q_{in}} = \frac{1}{C_f}$
- V_{out} is the amplitude of the output signal

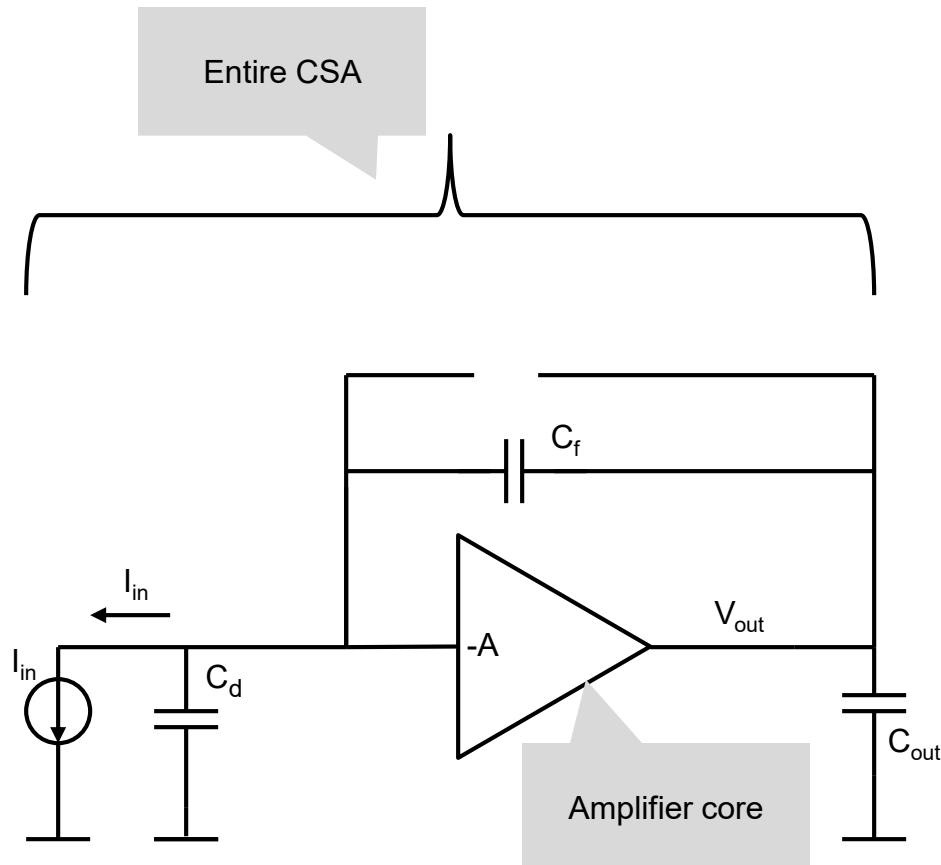

- Realistic CSA with R_f and C_f in feedback has the following transfer function (s is complex frequency):

- $$\frac{V_{out}(s)}{I_{in}(s)} = \frac{\alpha}{sC_f} \frac{1}{(sT_r+1)} \frac{sT_f}{(sT_f+1)} \equiv \frac{\alpha}{sC_f} H(s)_{LP} H(s)_{HP} \quad (1)$$



- Transfer function part $\frac{\alpha}{sC_f}$ describes the integrator

- $\frac{1}{(sT_r+1)}$ is the function of a low pass filter


- $\frac{sT_f}{(sT_f+1)}$ describes a high pass filter

- Therefore realistic CSA is a combination of an integrator with gain α/C_f , low pass- and high pass filter
- Such a CSA is an integrator and a filter in one component
- Factor α is equal to

  
- $$\alpha = \frac{\beta A}{1 + \beta A}, \text{ with } \beta = \frac{C_f}{C_f + C_d} \text{ and } A \text{ voltage amplification } (2)$$




 
- The response to charge pulse has two time constants, T_r and T_f
- T_r is the rise time constant and T_f is the fall time constant
- In a system with one time constant, the rise time from 0 to 95% of the maximum amplitude takes three time constants
- If $T_f \gg T_r$, the pulse has the asymmetric shape and $V_{\max} \sim \frac{\alpha Q}{sC_f}$





- Animation

 


 


 


 


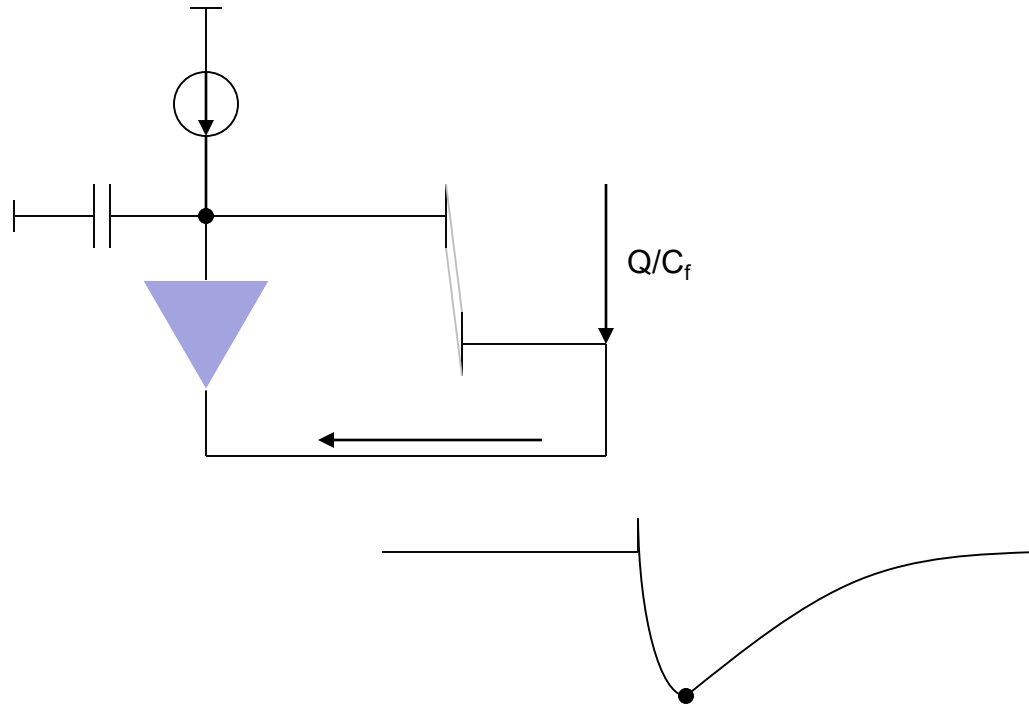

 


 

 


 


- Let us design CSA with the following specifications:
- Charge gain $V_{out,max}/Q_{in} = 1/2.5fF$
- The detector capacitance is $C_d = 100f$
- The capacitive load is $C_{out} = 1pF$
- We want that the amplification depends only on C_f : $A_Q = \frac{V_{out,max}}{Q_{in}} = \frac{\alpha}{sC_f} \sim \frac{1}{C_f} = \frac{1}{2.5fF}$ (3). Therefore $C_f = 2.5fF$ and $\alpha \sim 1$
- We specify $T_f = 2.5\mu s$
- Correct choice of T_r depends on the measurement we want to perform. If the aim is to measure amplitude, longer T_r is better (ideal for highest SNR is $T_r \sim T_f$)
- If time resolution should be optimized, the shortest possible T_r is better
- We specify $T_r \sim 50ns$

 


- How large should be amplification A ?
- To make amplification independent of other capacitances except C_f (specification (3)) factor $\alpha = \frac{\beta A}{1 + \beta A}$ (2) should be nearly 1. Therefore it should hold $\beta A \gg 1$. We chose $\beta A = 10$ (4)
- We will first calculate β : $\beta = \frac{C_f}{C_f + C_d} = \frac{2.5\text{fF}}{2.5\text{fF} + 100\text{fF}} \sim \frac{1}{40}$ (5)
- By substituting $\beta = 1/40$ into (5), we get $A = 400$
- How to achieve the specified time constants? Let us first take a look to T_f .
- For $\alpha \sim 1$, it holds $T_f = C_f R_f$
- We specified $T_f = 2.5\mu\text{s}$
- By substituting $T_f = 2.5\mu\text{s}$ into the formula for T_f , we obtain $R_f = 1\text{G}\Omega$

 

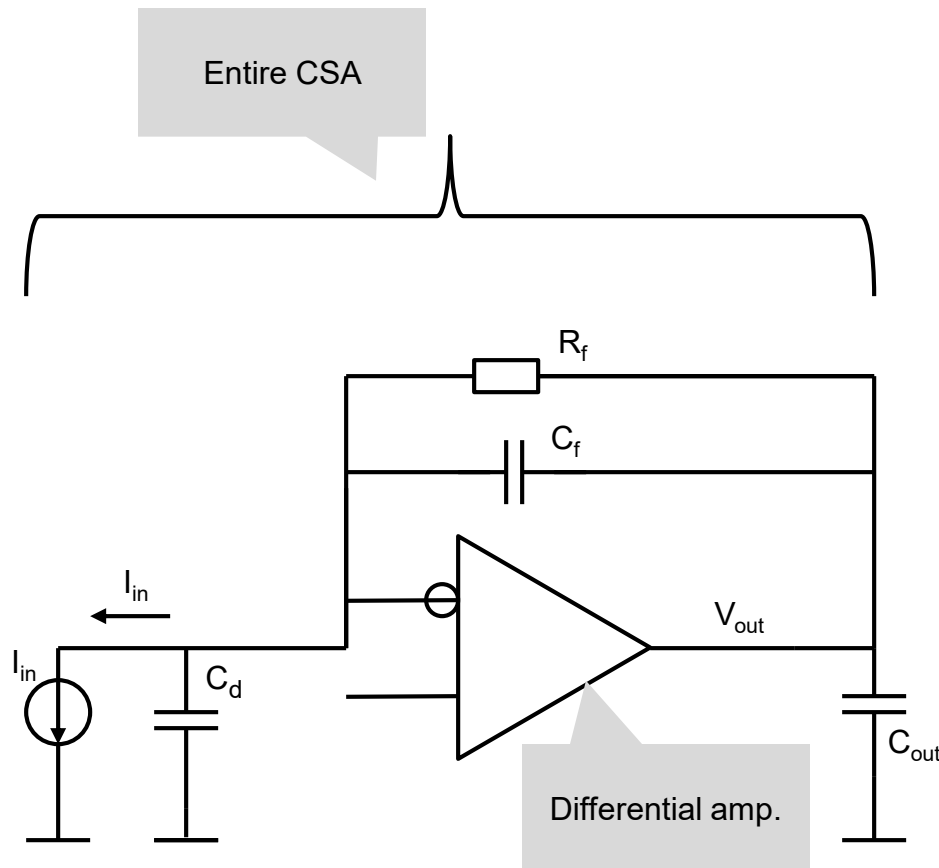
- Which amplifier type is suitable for the core part of the CSA?
- We chose differential amplifier for following reason:
- Differential amplifiers are less sensitive to noise and pickup in power lines – they have good power supply rejection ratio.
- We chose two-stage amplifier to achieve required open loop gain
- Such an amplifier is also called operational transconductance amplifier (OTA)




- The DC voltage gain of two stage operational transconductance amplifier (OTA) is:
- $A = A_1 \times A_2 = g_{m,in1} r_{out1} g_{m,in2} r_{out2}$ (6) with $r_{out1} = r_{ds,in1} \parallel r_{ds,load1}$; $r_{out2} = r_{ds,in2} \parallel r_{ds,load2}$
- If we substitute the simulated g_m and r_{ds} values ($g_{m,in1} \sim 70\mu S$, $g_{m,in2} \sim 50\mu S$, $r_{ds,pmos} = 800k\Omega$, $r_{ds,nmos} = 700k\Omega$) in (6), we obtain $A_1 \sim 25$, $A_2 \sim 20 \Rightarrow A \sim 500$
- DC gain is therefore large enough to assure $\alpha \sim 1$ (We obtain $\alpha \sim 0.93$, $\beta A = 12.5$)

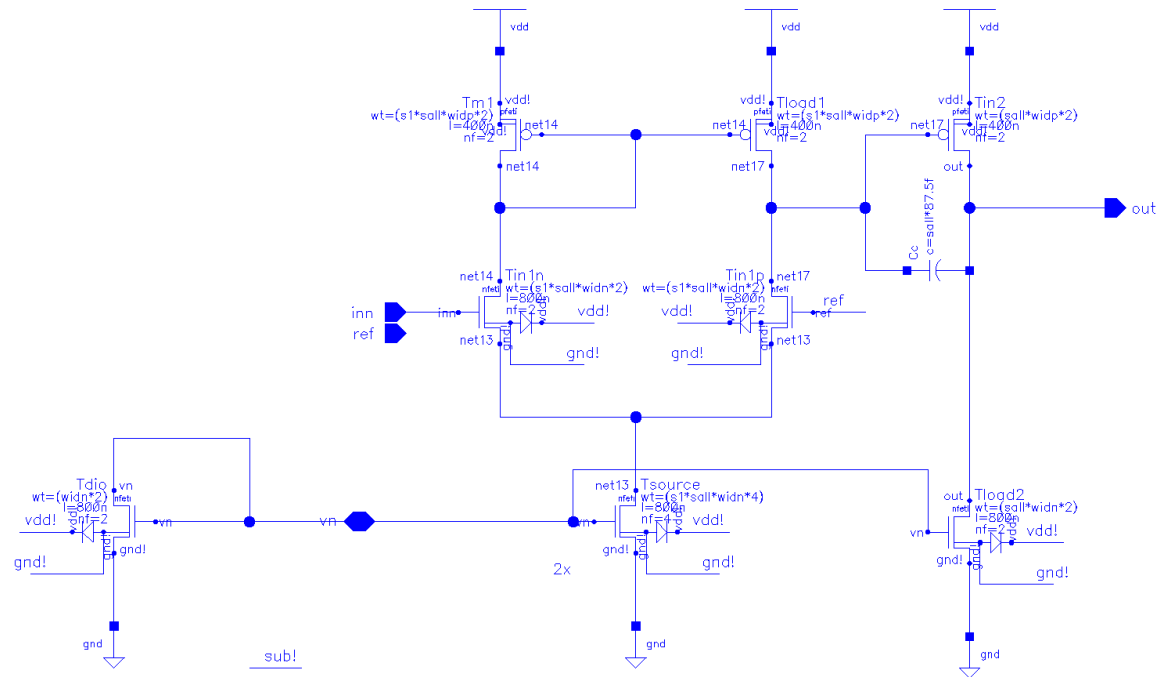

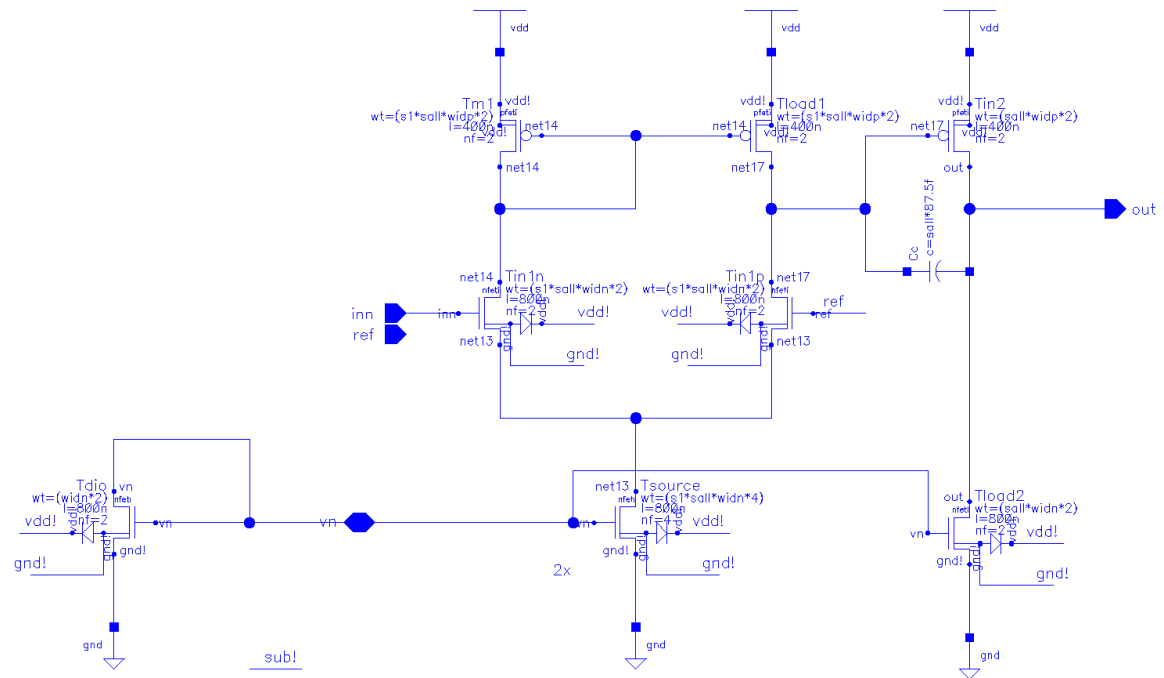- The rise time constant of the pulse response of the two stage amplifier is:
- $T_r = C_c / (g_{m,in1} \beta)$; $\beta = C_f / (C_d + C_f)$ (7)
- If we chose $C_c = 87.5fF$, we obtain from (7) $T_r \sim 50ns$



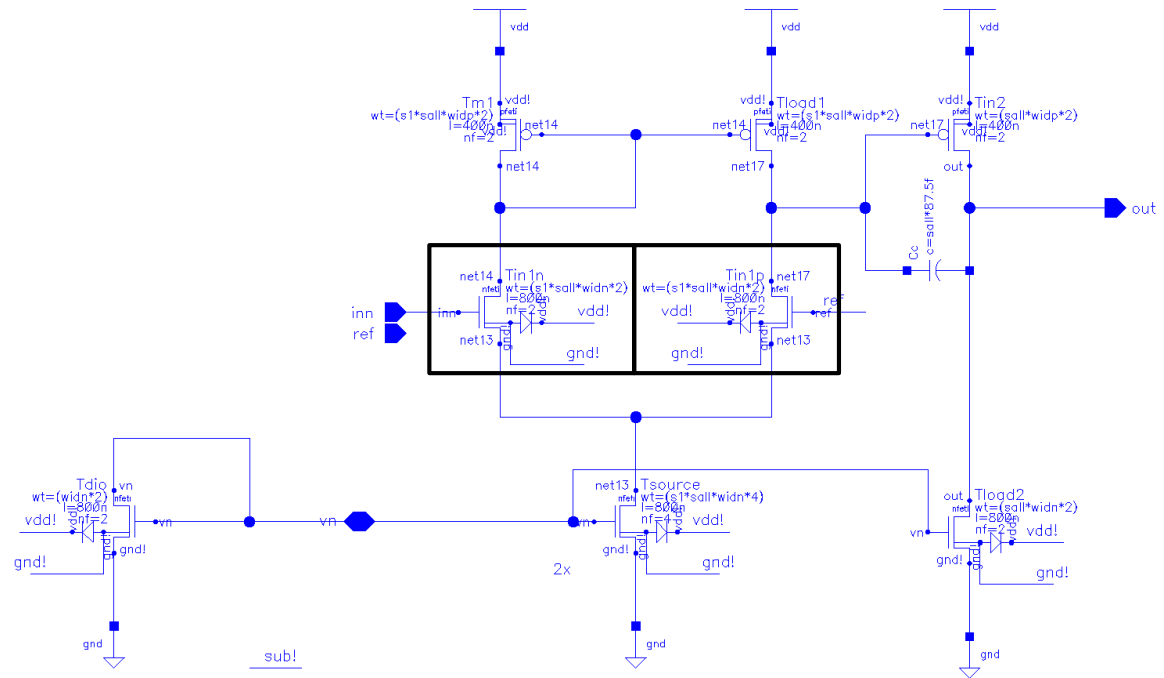
- The performance of electronic systems is limited by noise. Without noise, an amplifier would be able to detect arbitrarily small inputs.
- The main noise sources are 1) the input transistors of OTA T_{in1n} and T_{in1p} with its flicker- and thermal noise, 2) shot noise of detector leakage current and 3) the resistor R_f (thermal noise)



- The formula for equivalent noise charge (ENC¹) is:
- $$ENC^2 = \frac{1}{4} \left(2 \times (C_{det} + C_f)^2 \left(m k_f + \frac{S_{VT}}{T_r} \right) + S_{ID} T_f + S_{IR} T_f \right) \quad (8)$$
- The parameters are:
- S_{VT} is the power spectral density (PSD) for thermal noise of each input transistor. $S_{VT} = \frac{4kTn2/3}{g_m}$; with k Boltzmann constant, T absolute temperature and slope factor n ~ 1.25.
- S_{ID} is PSD of shot noise of detector leakage current I_{leak} : $S_{ID} = 2eI_{leak}$
- S_{IR} is PSD of thermal noise of R_f : $S_{IR} = \frac{4kT}{R_f}$
- k_f is coefficient of flicker noise for each input transistor. Power spectral density of flicker noise is k_f/f
- It can be derived: $k_f = \frac{\mu e^2 \langle n_{it} \rangle I_{dssat}}{L^2 n C'_{ox} g_m^2}$; with n_{it} density of traps that generate noise. Factor m is nearly $4 \times \frac{t_{peak}}{T_r} \sim 16$
- Notice factor “2 ×” in eq. (8) because there are two input transistors, whose noise power adds
- **Questions:**
- Which noise component gets large for fast amplifier (T_r small)?
- Which noise components get smaller when we increase the widths and currents of all transistors, without changing T_r ?

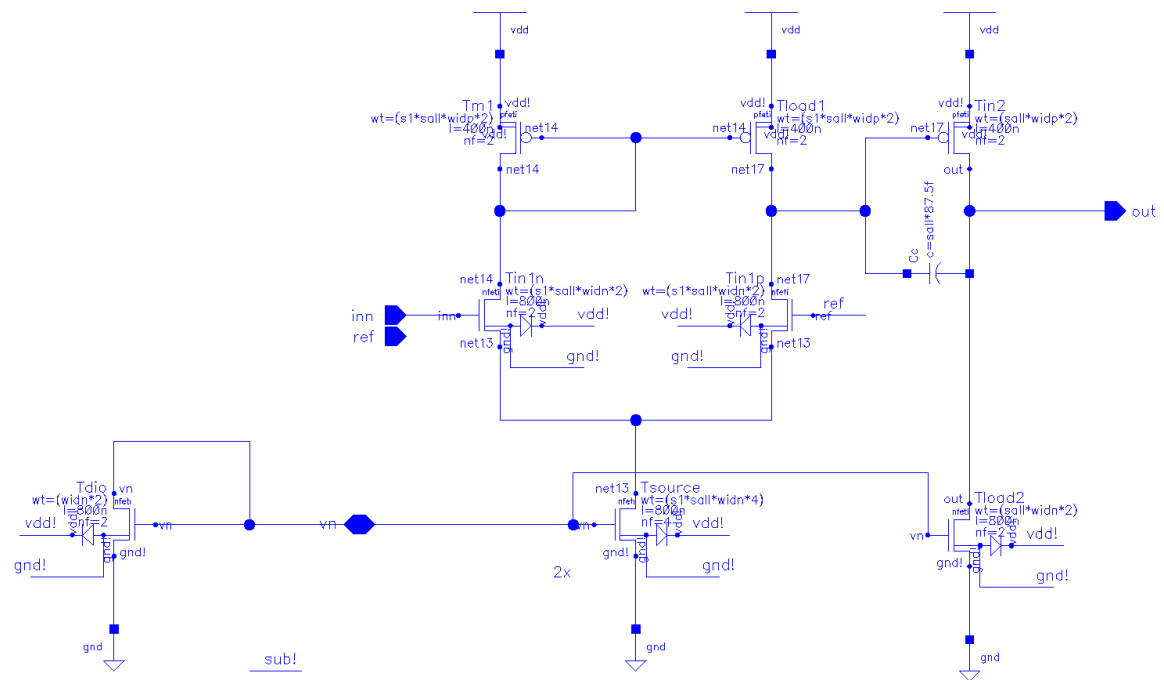1: ENC is the input signal that produces the output amplitude equal to root mean square (RMS) of noise


- We have fulfilled the specifications for current, gain and time constant. Let us now optimize the amplifier to have lowest possible noise.
- To optimize the amplifier, we could 1) scale up the transistor widths in the first stage (parameter s1), 2) scale up the widths in the second stage, 3) scale up C_c and 4) scale up all transistor widths and C_c (parameter sall)




MOSFET

Metal oxide semiconductor field effect transistor

 
- The state of the transistor is described by two voltages – V_{gs} and V_{ds} and by two currents I_{ds} and I_{gs} .
- Gate represents only a capacitance, no DC current flows




- I_{ds} - V_{ds} characteristics for different V_{gs} – e.g. 100mV, 200mV...
- In the right line region, the current is relatively independent of V_{ds} – we call it the saturation region
- Ideally: $I_{ds} = I_{dssat}$ for all $V_{ds} > V_{dssat}$
- In the left line region, the current drops to 0. We call this region the triode range. For small V_{ds} , the current-voltage dependence is approximately linear (linear range)

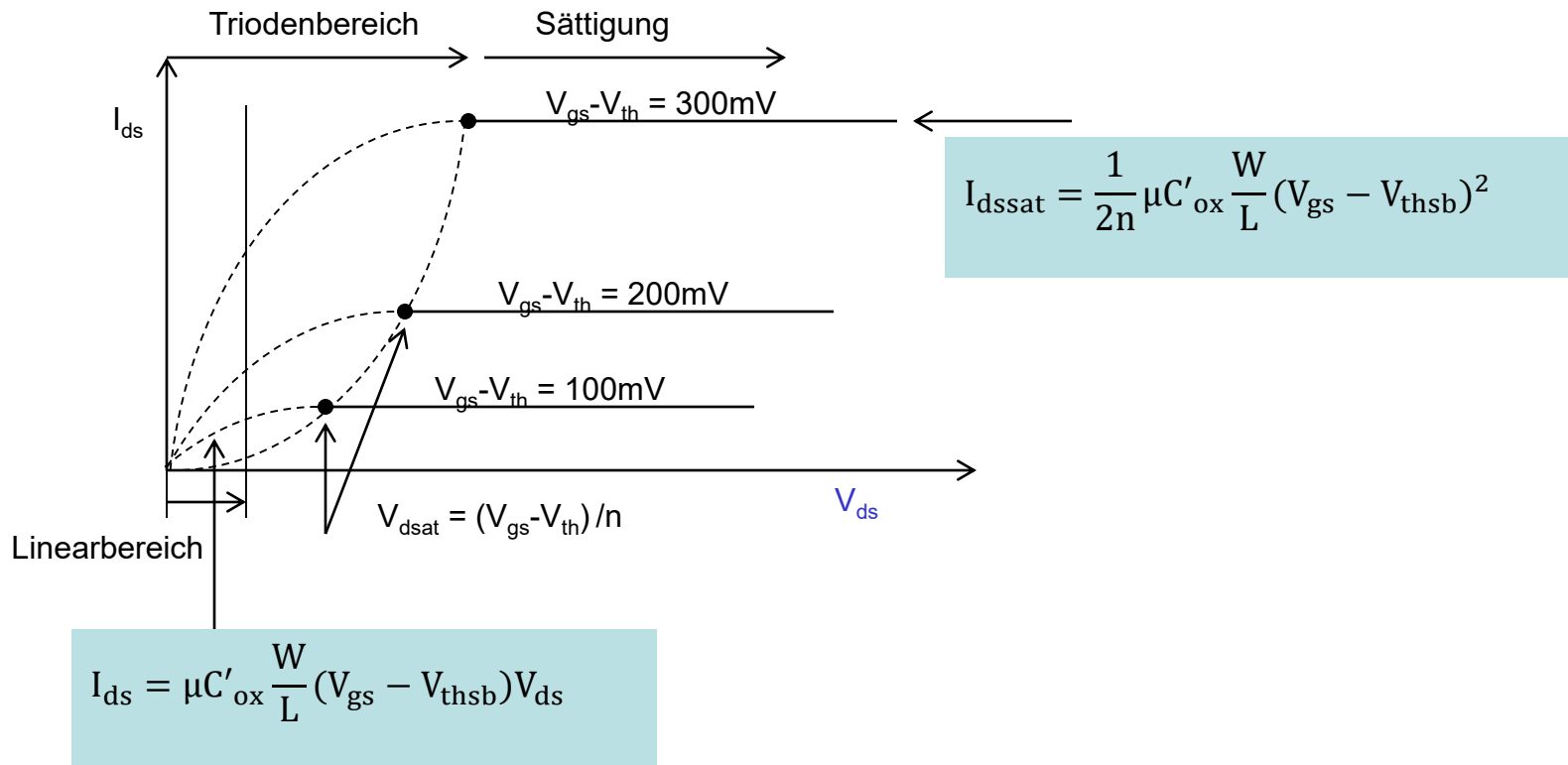


 
- Current in saturation depends quadratically on V_{gs}
- $I_{dssat} = \frac{1}{2n} \mu C'_{ox} \frac{W}{L} (V_{gs} - V_{thsb})^2$
- At the boundary between the saturation and triode region holds: $V_{ds} = V_{dssat} = (V_{ds} - V_{thsb})/n$
- In the saturation range, the transistor behaves like a voltage-controlled current source



- $I_{ds}-V_{gs}$ characteristic

 

  - The input characteristic is linearized in the area around the operating point -> small signal model
- The slope of the line $g_m = dI_{dssat}/dV_{gs}$ is called transconductance.
- For the small signals, the linear models are used



$$g_m = \frac{dI_{dssat}}{dV_{gs}}$$




$$I_{dssat} = \frac{1}{2n} \mu C'_{ox} \frac{W}{L} (V_{gs} - V_{thsb})^2$$

$$I_{dssat} = \frac{k}{2} \frac{W}{L} (V_{gs} - V_{thsb})^2$$

$$g_m = \sqrt{2kI_{dssat} \cdot (W/L)}$$

Small signal model

- $I_{ds} = I_{dssat}(V_{gst}) \left(1 + \frac{V_{ds} - V_{dssat}}{V_A} \right)$; $v_{gst} = V_{gs} - V_{thsb}$; $V_{thsb} = V_{th} - (n - 1)V_{bs}$
- $V_{dssat} = (V_{ds} - V_{thsb})/n$
- Small signal. The equation can be decomposed into DC and AC part
- $i_{DS} = I_{ds,DC} + i_{ds,ac}$
- $i_{ds,ac} = \frac{dI_{ds}}{dV_{gs}} v_{gs} + \frac{dI_{ds}}{dV_{ds}} v_{ds} + \frac{dI_{ds}}{dV_{sb}} v_{bs}$
- $= g_m v_{gs} + g_{ds} v_{ds} + g_{mb} v_{bs}$

 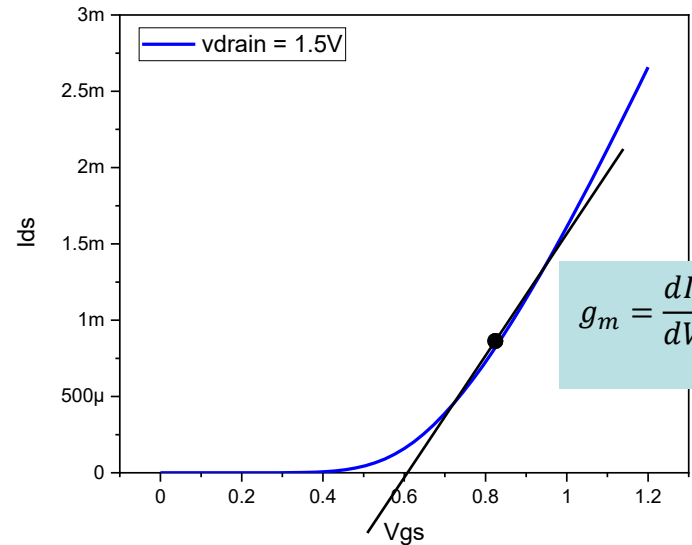 


Basic analog circuits

Basic analog circuits

Current source


 
- Voltage-controlled current source (U-I converter)
- Signal voltage is at the gate
- Drain is connected to bias voltage to assure transistor saturation. Condition: $V_{ds} > V_{dssat}$
- It holds
- $I_{out} = \frac{1}{2n} \mu C'_{ox} \frac{W}{L} (V_{in} - V_{thsb})^2$; n is the slope factor $n \sim 1.25$; V_{thsb} is the threshold voltage $V_{thsb} = 0.5V + (n-1) V_{sb}$



Basic analog circuits

Diode-connected transistor

  
- $V_{ds} = V_{gs} > \frac{v_{gs} - v_{thsb}}{n} \equiv V_{dssat}$
- deshalb
- $I_{ds} = I_{dssat}$
- $I_{dssat} = \frac{1}{2n} \mu C'_{ox} \frac{W}{L} (V_{gs} - V_{thsb})^2$



Basic analog circuits

Current mirror


- A current mirror is the combination of a MOSFET diode and a current source
- $I_{in} = k_s \frac{W_{dio}}{L_{dio}} (V_{gsdio} - V_{th})^2 \left(1 + \frac{V_{dsdio} - V_{dssat}(V_{gsdio})}{V_A}\right)$
- $V_{dsdio} = V_{gsdio} = V_{in}$ (diode short)
- $I_{out} = k_s \frac{W_{out}}{L_{out}} (V_{gsout} - V_{th})^2 \left(1 + \frac{V_{dsout} - V_{dssat}(V_{gsout})}{V_A}\right)$
- $V_{gsdio} = V_{gsout} = V_{in}$ (gate connection); $V_{dsout} = V_{out}$ (definition)
- **Condition 1:** T_{out} in saturation and
- **Condition 2:** $V_A \gg V_{ds} - V_{dssat}$ or $V_{in} \sim V_{out}$

 

$$\frac{I_{out} = k_s \frac{W_{out}}{L_{out}} (V_{in} - V_{th})^2}{I_{in} = k_s \frac{W_{dio}}{L_{dio}} (V_{in} - V_{th})^2}$$

$$I_{out} = I_{in} \frac{\left(\frac{W_{out}}{L_{out}}\right)}{\left(\frac{W_{dio}}{L_{dio}}\right)}$$

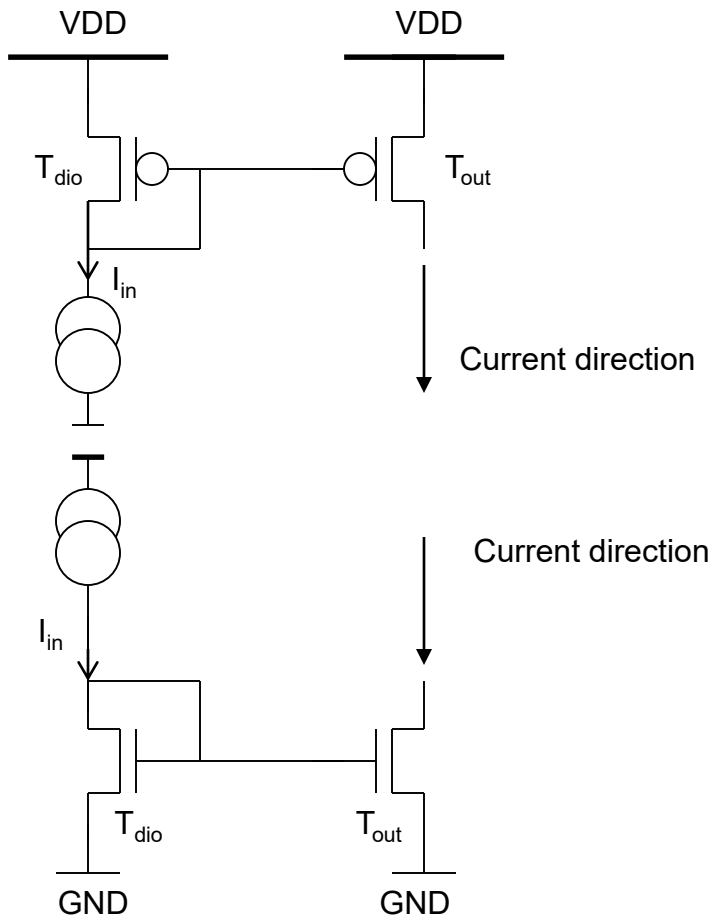
- PMOS current mirror: Source connected to VDD (positive power supply), current flows "to the outside"
- NMOS current mirror: Source connected to GND, current direction inwards




Basic analog circuits

Common source amplifier with resistor

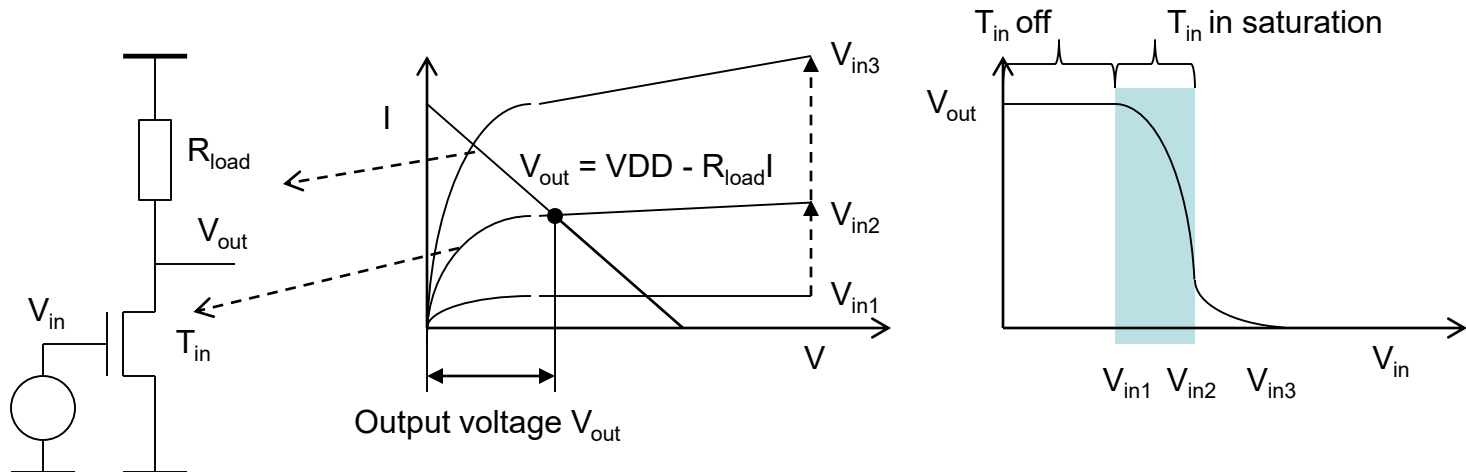- We can derive the characteristic curve mathematically (with the help of equations) or graphically (with the help of characteristic curves).
- Load line analysis



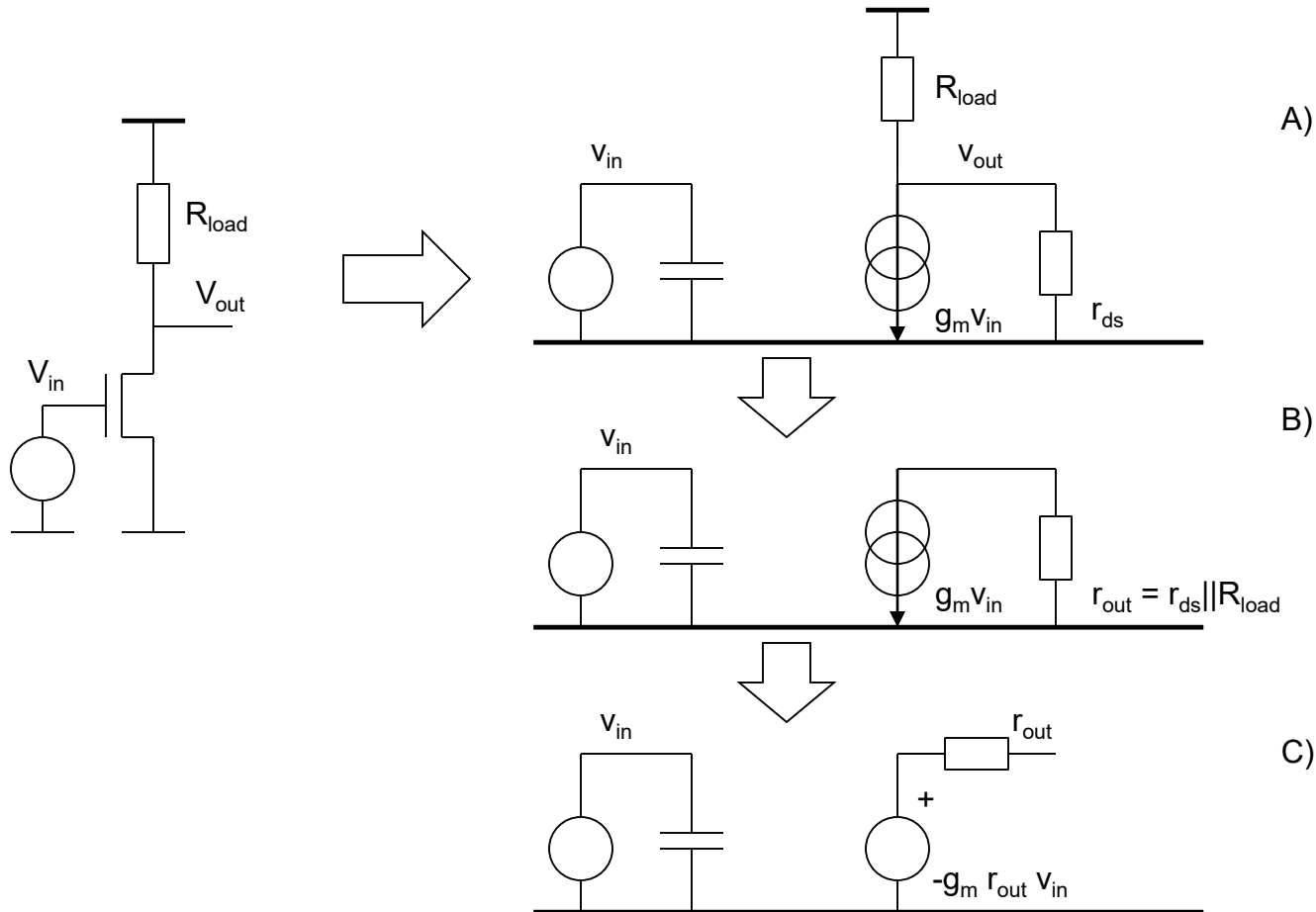- For the working area where T_{in} is in saturation (condition is $V_{out} > V_{dssat} = V_{in} - V_{th}$), we can draw the small signal circuit.
- The voltage amplification is :
- $A = v_{out}/v_{in} = -g_m (r_{ds} \parallel R_{load})$




Basic analog circuits


Common source amplifier with active load

- To maximize amplification, we need relatively large values for g_m and r_{out} .
- The disadvantage of the amplifier with a linear resistor is that you cannot maximize both g_m and $r_{out} = R_{load} \parallel r_{ds}$.
- Why?
- $r_{ds} = \frac{E_{sat}L}{I_{dssat}}$
- $g_m \sim I_{dssat}$

 
If the resistance R_{load} is large, its characteristic curve is close to the X-axis. The transistor current is then small. A small current leads to a small transconductance




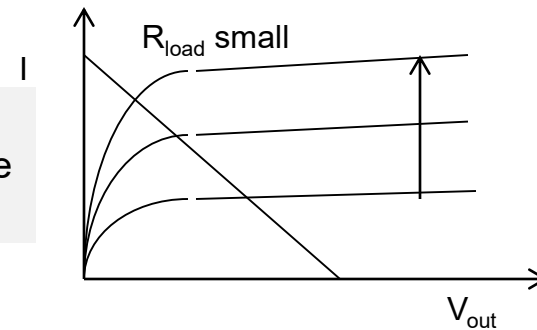
If R_{load} is small, the characteristic curve increases. The transistor current and g_m are higher. However, because of the small R_{load} , the gain is small.



 - A load characteristic curve that rises relatively quickly and then runs horizontally in the large area would be better than the characteristic curve of linear resistor.




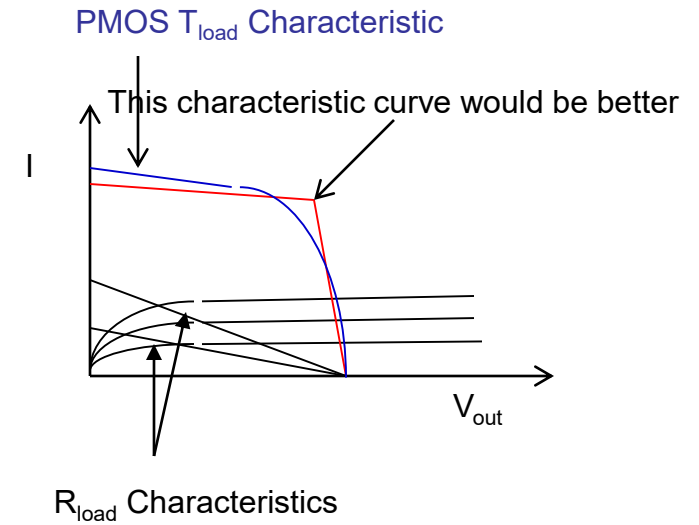 - A PMOS current source has an almost ideal characteristic curve




- We get a better amplifier when we replace resistor R_{load} with a PMOS current source
- A load element realized with a transistor is called active load

Bias circuit

 

 
Simple implementation of the bias circuit



Bias circuit for the current source in the form of MOSFET diode and a current source.


Feedback

- An important technique that turns the non-ideal active components into good linear amplifiers is negative feedback. Feedback enables the design of precise amplifiers and oscillators
- Feedback: Automatic regulation of the voltage v_{IN} to the “threshold”
- FB allows, in addition to control, also signal amplification
- $v_{IN} = A_{IN}v_S + \beta v_O$
- $v_{IN} = \text{const}$ (Regelung)
- $dv_O = \frac{-A_{IN}}{\beta} dv_S \equiv dv_S$ AFB


 


Differential amplifier


- Differential amplifiers

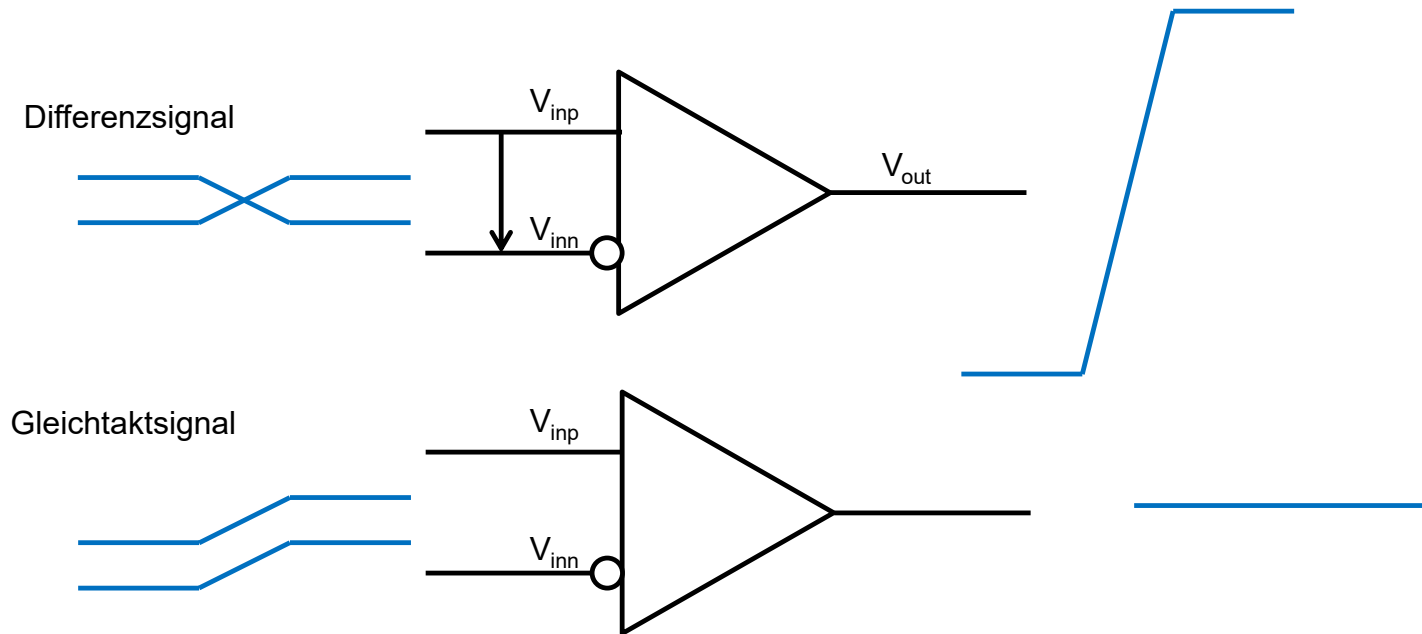

- Differential amplifiers

  



Small signal model with a current source

 

Small signal model with a voltage source

Layout

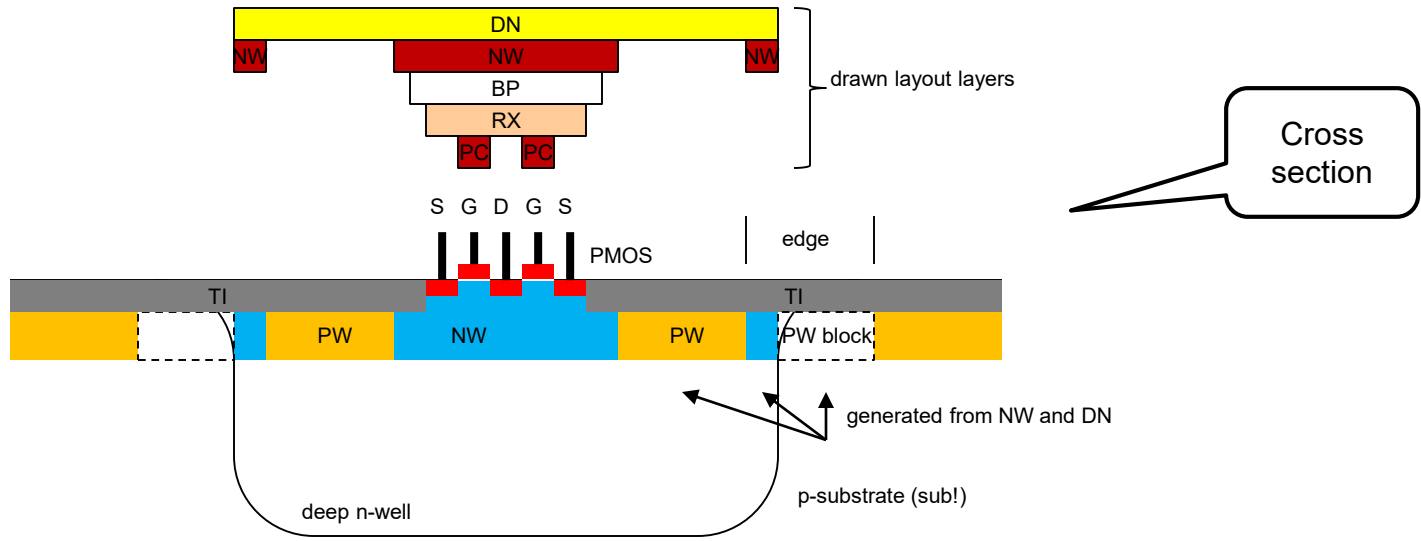

 


drawn layout layers



Cross section







Si substrate
Cross section


 




Top view

 
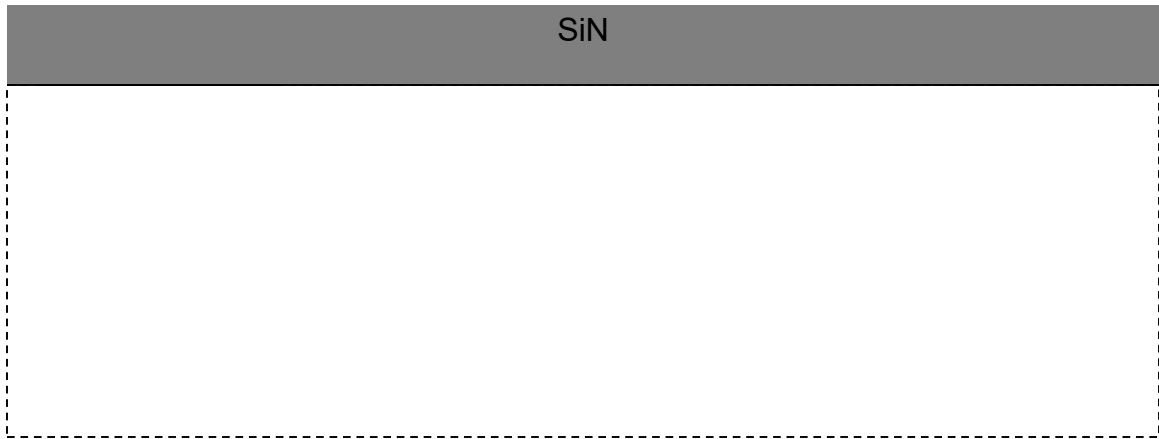


 
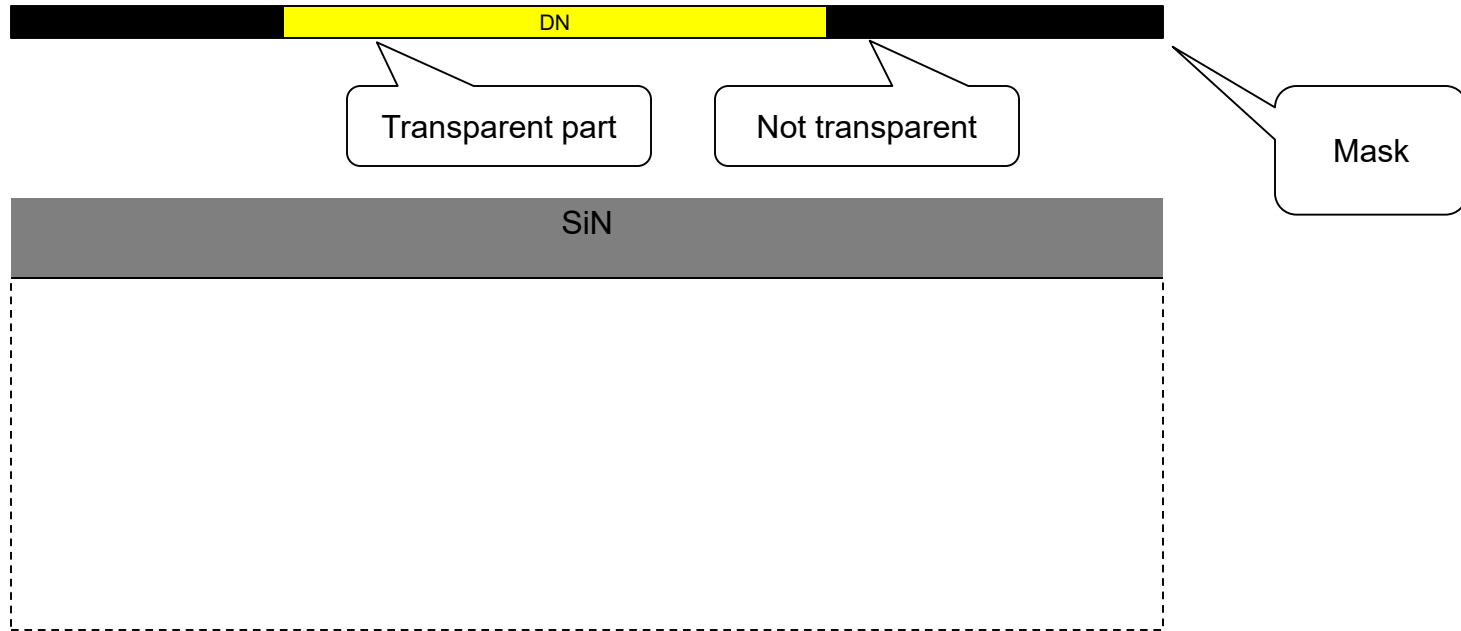


 
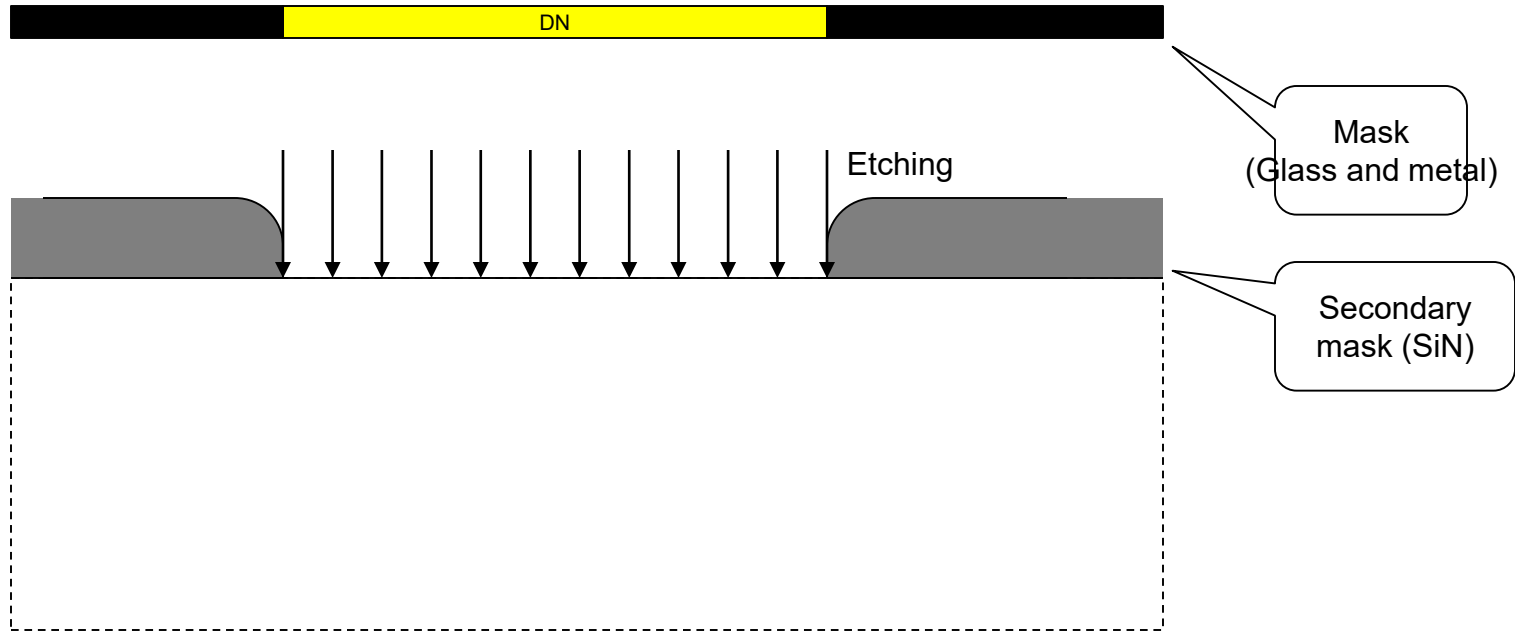


  


 
 


 
 


 
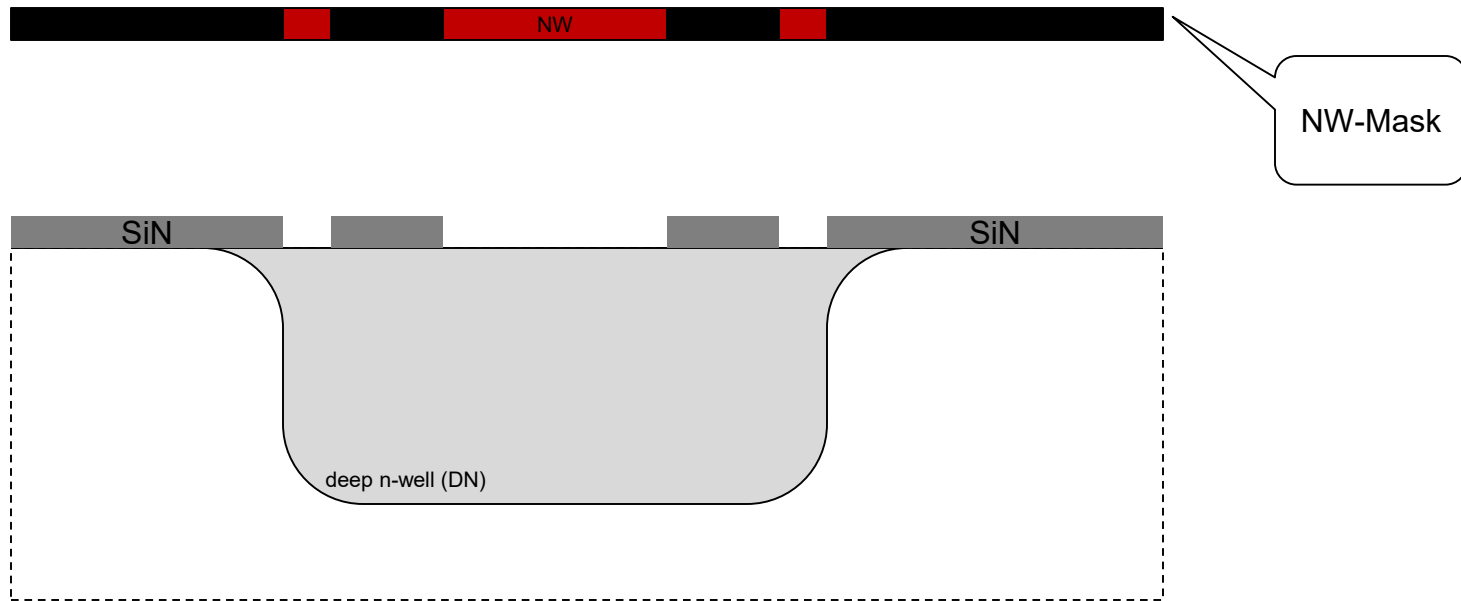


  


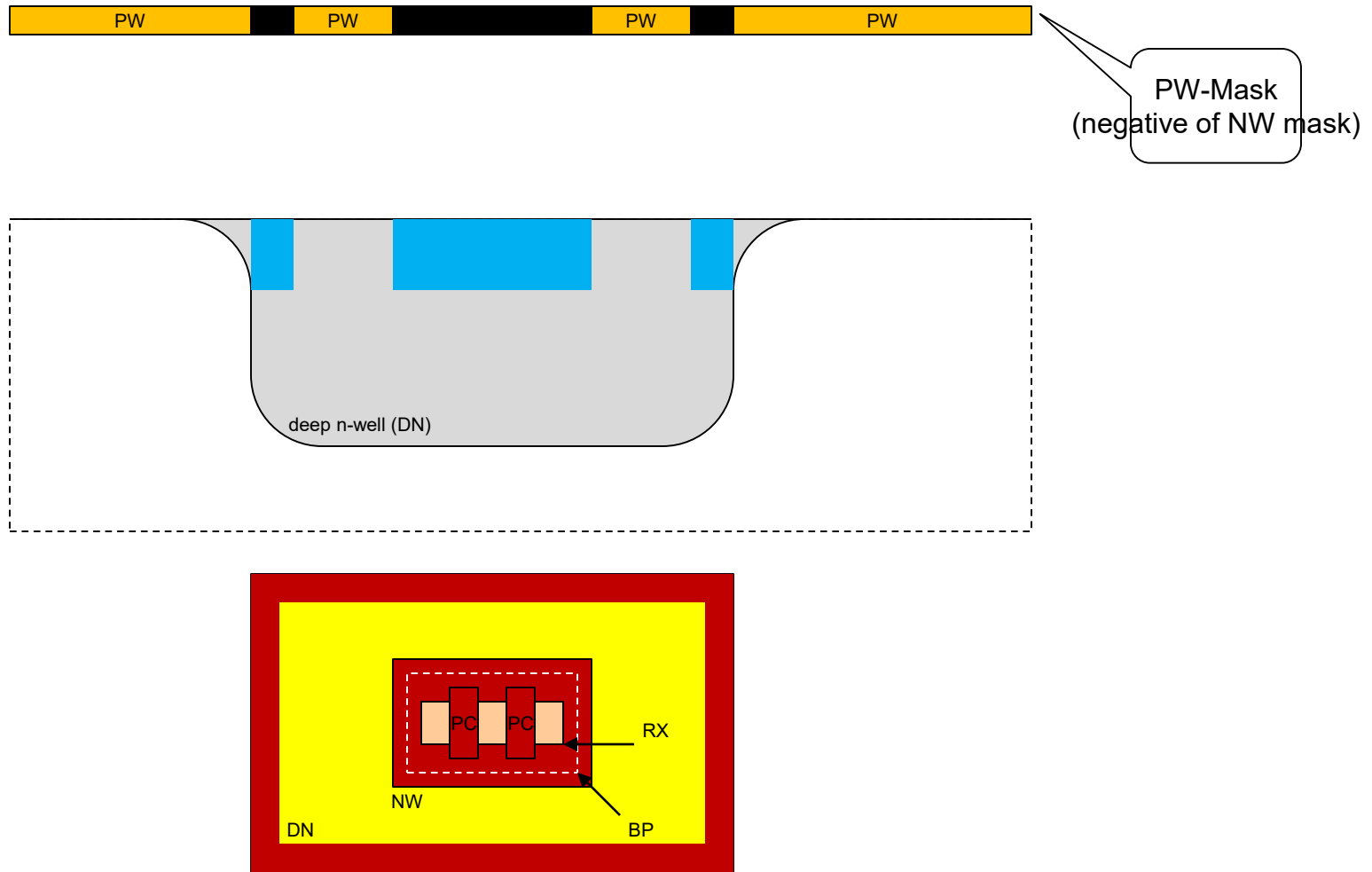

 
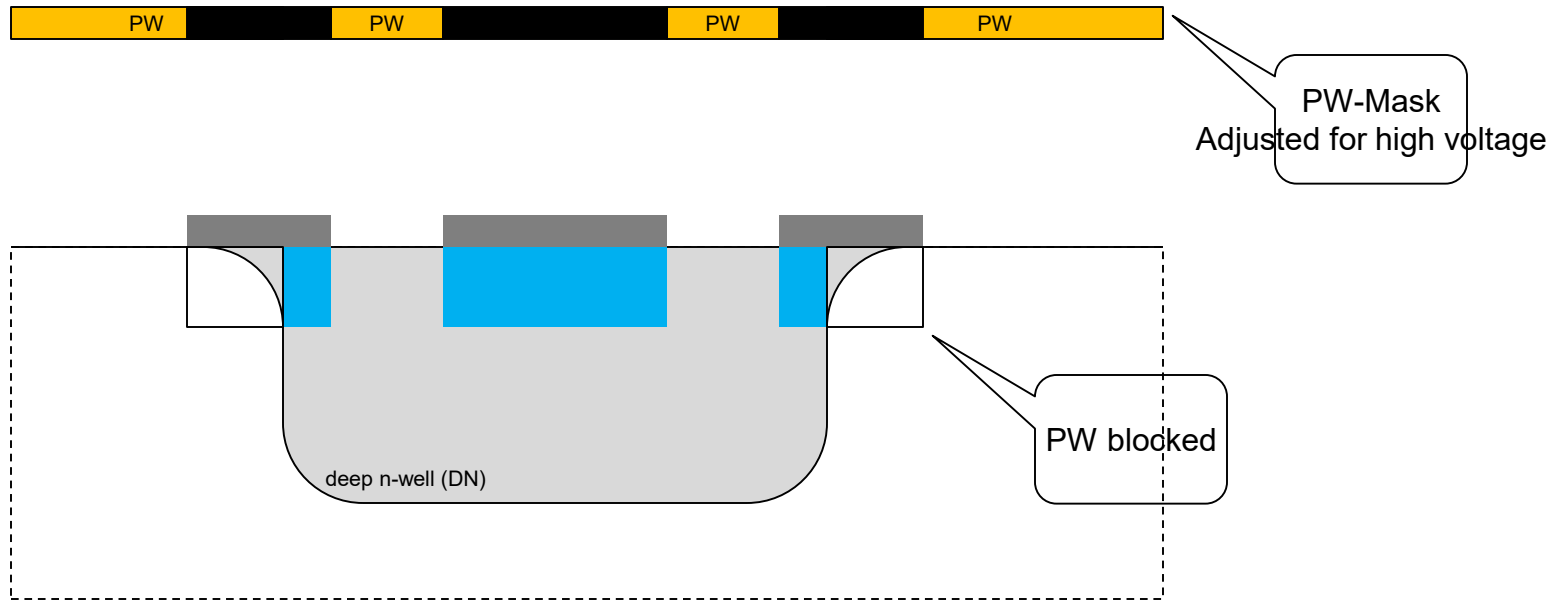


  

  


 


RX-Mask defines active regions

 
 






Etching of a trench

 
 


  Trench filled with oxide (trench isolation)



 
 
Gate oxide is formed by thermal oxidation



  



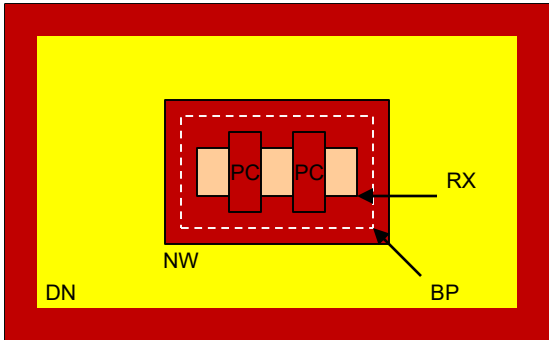 Polysilicon-contacts (PC) formed by deposition





BP mask defines p+ doped layers

